
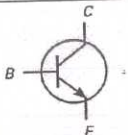
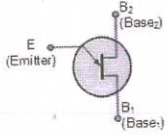
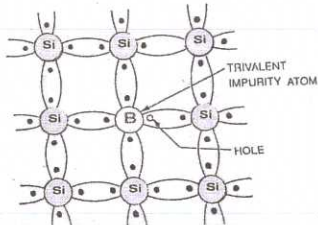
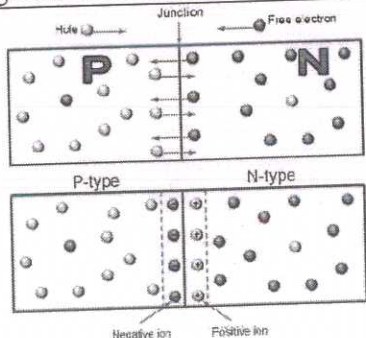
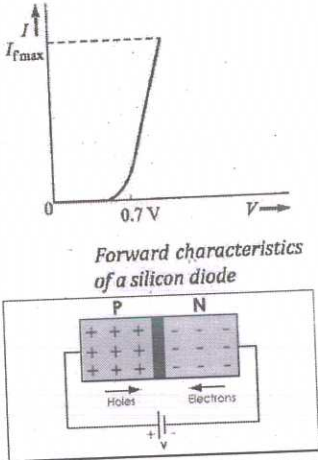
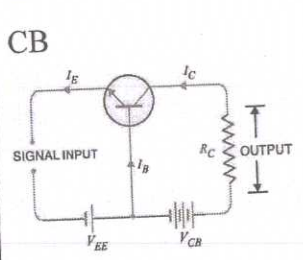
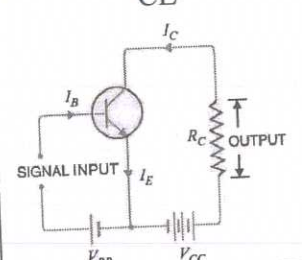
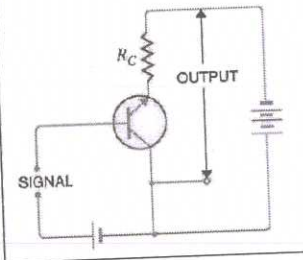
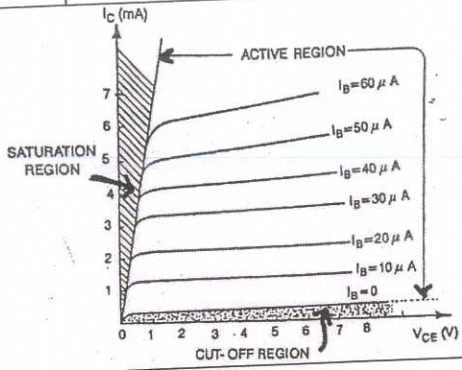



**SCORING INDICATORS**

Course Code: 2041		Revision : 2021	SET 1		
Course Title : BASIC ELECTRONICS		QID : 2106220058			
Qn. No.	Scoring Indicator	Split score	Sub Total	Total Score	
<b>PART A</b>					9
I.1	The process of adding impurities to the semiconductor materials is called doping.	1	1	1	
I.2	0.6 V or 0.7 V	1	1	1	
I.3		1	1	1	
I.4	$\gamma$ is the ratio of transistor's emitter current to base current.	1	1	1	
I.5	Cut off	1	1	1	
I.6		1	1	1	
I.7	Drain current is controlled by gate voltage.	1	1	1	
I.8	Ripples at the output of a rectifier can be removed by filter circuits.	1	1	1	
I.9	In order to achieve good differentiation, the time constant RC of the circuit should be much smaller than the time period of the input wave.	1	1	1	
<b>PART B</b>					24
II 1	<b>Diagram - P type</b>  <p>When a trivalent impurity is added to silicon (or germanium), impurity atom replaces a silicon atom in its crystalline structure. Boron atom has three valence electrons- These electrons form covalent bonds with the three neighbouring silicon atoms - The fourth neighbouring silicon atom is unable to form a covalent bond - There is a deficiency of an electron around the boron atom</p>	1	3	3	
II 2	Drift current is due to the motion of charge carriers due to the force exerted on them by an electric field. Diffusion current flows as a result of a gradient of carrier concentration. A gradient of carrier concentration arises near the boundary of a PN-junction	1.5	3	3	
II 3		1.5	3	3	

	Density gradient across the junction results in majority carrier diffusion across the junction. Free electrons in the N region begin to diffuse across the junction into the P region where they combine with holes near the junction. This process creates a layer of two ions creating a voltage barrier.	1.5														
II 4	 <p>Forward characteristics of a silicon diode</p>	1.5	3	3												
II 5	<table border="1" style="width: 100%; text-align: center;"> <thead> <tr> <th>Emitter junction</th> <th>Collector junction</th> <th>Region of operation</th> </tr> </thead> <tbody> <tr> <td>Forward biased</td> <td>Reverse biased</td> <td>Active</td> </tr> <tr> <td>Forward biased</td> <td>Forward biased</td> <td>Saturation</td> </tr> <tr> <td>Reverse biased</td> <td>Reverse biased</td> <td>Cutoff</td> </tr> </tbody> </table>	Emitter junction	Collector junction	Region of operation	Forward biased	Reverse biased	Active	Forward biased	Forward biased	Saturation	Reverse biased	Reverse biased	Cutoff	3	3	3
Emitter junction	Collector junction	Region of operation														
Forward biased	Reverse biased	Active														
Forward biased	Forward biased	Saturation														
Reverse biased	Reverse biased	Cutoff														
II 6	<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>CB</p>  </div> <div style="text-align: center;"> <p>CE</p>  </div> <div style="text-align: center;"> <p>CC</p>  </div> </div>	3	3	3												
II 7		3	3	3												
II 8	 <p>Low resistance in input circuit, lets any small change in input signal to result in an appreciable change in the output. The emitter current caused by the input signal contributes the collector current, which when flows through the load resistor <math>R_L</math>, results in a large voltage drop across it. [CE configuration can also be used for explanation]</p>	2	3	3												
		1														

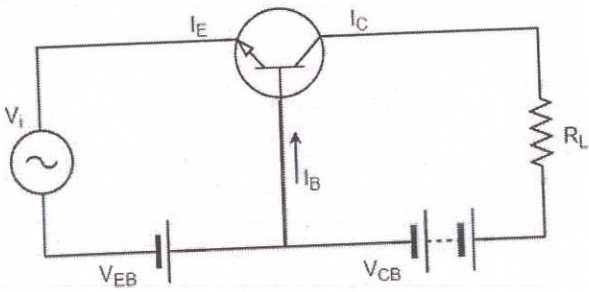


Semiconductor

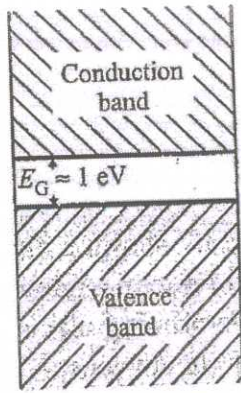

Semiconductors

The forbidden energy gap is not wide. The energy provided by heat at room temperature is sufficient to lift electrons from the valence band to the conduction band. Some electrons jump the gap and go to the conduction band. At room temperature, semiconductors are capable of conducting some electric current. At absolute zero temperature semiconductor acts like a perfect insulator.


Insulator

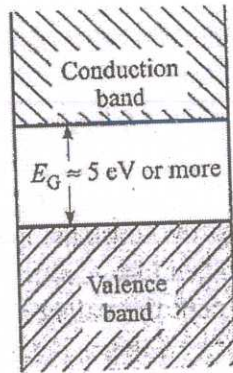

Insulators

Very wide forbidden energy gap (5 eV or more) - Valance electrons are bound tightly - practically impossible for an electron in the valence band to jump the gap to reach the conduction band - Only at very high temperatures or under very stressed (electrically) conditions, an electron can jump the gap - At room temperature, an insulator does not conduct because there are no conduction electrons in it

III 3.

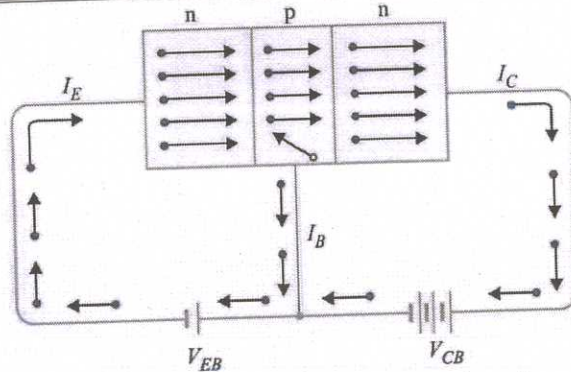

EB junction is forward biased while CB junction is reverse biased - electrons in the emitter are pushed towards the base constituting  $I_E$  - these electrons enter the p-type material, tend to combine with holes - only a few electrons combine with holes to constitute base current  $I_B$  - remaining electrons diffuse across the base region and reach the collector and are collected by the collector - This constitutes collector current  $I_C$   
 $I_E = I_B + I_C$

III 4. Current amplification factor ( $\alpha$ ) in CB

It is the ratio of output current to input current in CB configuration

$$\alpha = \frac{I_C}{I_E}$$

Base current amplification factor ( $\beta$ ) in CE

It is the ratio of output current to input current in CE configuration

$$\beta = \frac{I_C}{I_B}$$

Relation between  $\alpha$  and  $\beta$

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \dots \dots (1)$$

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E} \dots \dots (2)$$

$$\bullet I_E = I_B + I_C \dots \dots (3)$$

$$\bullet \Delta I_E = \Delta I_B + \Delta I_C \dots \dots (4)$$

Dividing eqn 4 by  $\Delta I_C$

$$\bullet (\Delta I_E / \Delta I_C) = (\Delta I_B / \Delta I_C) + (\Delta I_C / \Delta I_C)$$

$$\bullet (1/\alpha_{ac}) = (1/\beta_{ac}) + 1$$

Rearranging the equations, we get

$$\alpha_{ac} = \frac{\beta_{ac}}{1 + \beta_{ac}}$$

$$\bullet \text{and } \beta_{ac} = \frac{\alpha_{ac}}{1 - \alpha_{ac}}$$

$$\bullet \text{Similarly } \alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}} \text{ and } \beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$

1

4


1  
[eqn]

4

7

7


III 5.

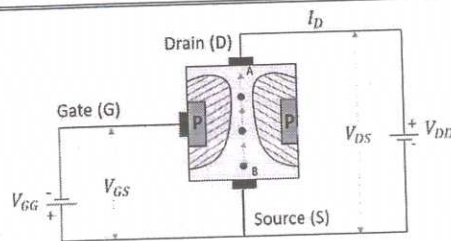

When a voltage  $V_{DS}$  is applied between drain and source terminals and voltage on the gate is zero, the two pn junctions at the sides of the bar establish depletion layers. The electrons will flow from source to drain through a channel between the depletion layers. When a reverse voltage  $V_{GS}$  is applied, the width of the depletion layers is increased. This reduces the width of conducting channel, thereby increasing the resistance of n-type bar. Consequently, the current from source to drain is decreased.

3

III 6.

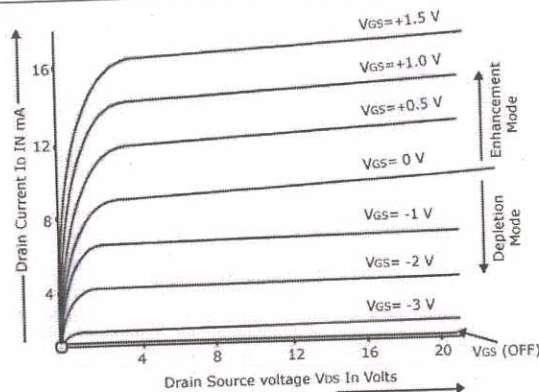


Upper curves are for positive  $V_{GS}$  and the lower curves are for negative  $V_{GS}$ . The bottom drain curve is for  $V_{GS} = V_{GS(OFF)}$ . For a specified  $V_{DS}$ ,  $V_{GS(OFF)}$  is the gate-source voltage at which drain current reduces to a certain specified negligibly small value. For  $V_{GS}$  between  $V_{GS(OFF)}$  and zero, the device operates in depletion-mode while for  $V_{GS}$  exceeding zero the device operates in enhancement mode. These drain curves display an ohmic region, a constant-current source region and a cut-off region

3

III 7.	BJT	FET	7 [any 7]	7	7
	Bipolar	Unipolar			
	Operation depends on both majority charge carriers and minority charge carriers.	Operation depends on majority charge carriers			
	Input impedance very less	Input impedance is very large.			
	Current control device.	Voltage-controlled device.			
	Noisy	Less noisy.			
	Less temperature stability	Better temperature stability.			
	Cheaper.	costlier than BJT			
	It has more gain.	It has less gain.			
	Bigger in size	Smaller in size			
	Its switching time is medium.	Its switching time is fast.			
	It consumes more power.	It consumes less power			

III 8.

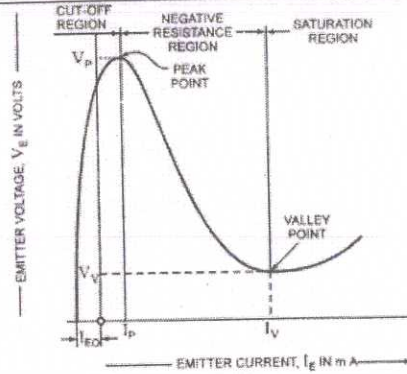


Static Emitter-Characteristic For a UJT





Emitter firing potential is given by  $V_P = \eta V_{BB} + V_B$

When  $V_E$  becomes equal to  $\eta V_{BB}$ , neither reverse nor forward current will flow. When  $V_E = V_P$ , emitter current  $I_E$  starts to flow through  $R_{B1}$  to ground, that is B1. This is the minimum current that is required to trigger the UJT. This is called the peak-point emitter current and denoted by  $I_P$ . when the emitter diode starts conducting, charge carriers are injected into the  $R_{B1}$  region of the bar. Resistance of region  $R_{B1}$  decreases rapidly due to additional charge carriers. With this decrease in resistance, the voltage drop across  $R_{B1}$  also decrease, causing the emitter diode to be more heavily forward biased, in turn, results in larger forward current and consequently more charge carriers are injected causing still further reduction in the resistance of the  $R_{B1}$  region. Thus the emitter current goes on increasing. Since  $V_A$  decreases with the increase in emitter current, the UJT is said to have negative resistance characteristic.

III 9.

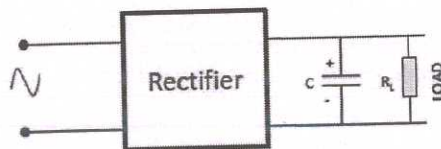

AC components in the rectifier output find a low reactance path through capacitor - C gets charged when the diode (in the rectifier) is conducting - C gets discharged through  $R_L$  when the diode is not conducting - The stored energy in the capacitor maintains the output voltage at a high value for a long period - So the ripple voltage is minimized

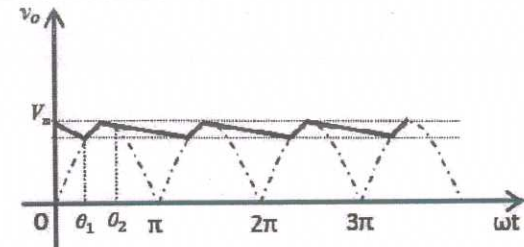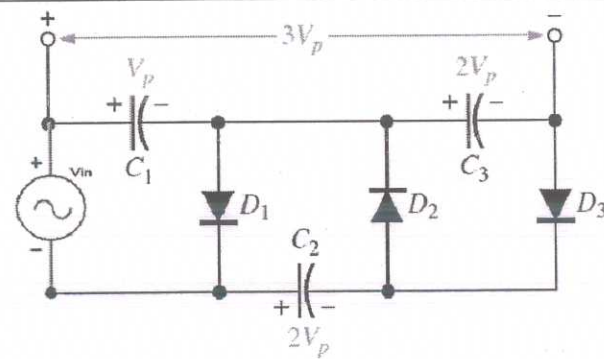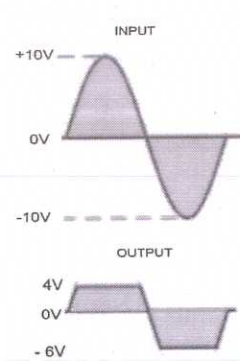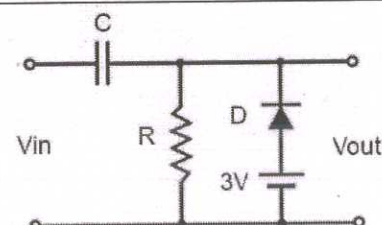		2		
III 10.	 <p>During the first positive half cycle of the input C1 charges to the peak value of the input voltage <math>V_p</math> - During the negative half cycle, D2 is forward biased diodes D1 and D3 are reverse biased - C2 is charged to twice the peak voltage of the input signal (<math>2V_p</math>) - During the second positive half cycle, the D3 is forward biased, diodes D1 and D2 are reverse biased - C3 is charged to <math>2V_m</math> - Output voltage is taken across capacitors C1 and C3</p>	4	7	7
III 11.	 <ul style="list-style-type: none"> <li>- When the input voltage is greater than 4V, D1 is forward biased and D2 is reversed biased - limits the output voltage at 4V</li> <li>- When the input voltage is less than -6V, D2 is forward biased and D1 is reversed biased - limits the output voltage at -6V</li> <li>- When the input voltage is between 4V and -6V, both the diodes are reversed biased - During this time, output=input</li> </ul>	4	7	7
III 12.	 <p>During negative cycle of input, C charges through diode and dc source till <math>(V1+3)</math> volts with positive polarity of the capacitor at right. Charging is limited to <math>(V1+3)</math>. Capacitor acts as a dc source in series with the input. Then output = <math>(V1+3) + \text{input}</math></p>	4	7	7