
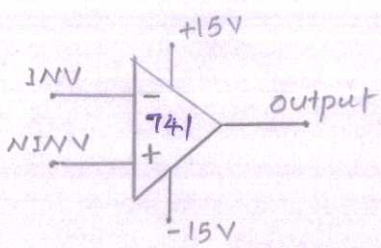


Qst No.	Scoring Indicator.	Split up Score	Sub Total	Total
<b>PART - A</b>				
I 1.	Maximum rate of change of output voltage with respect to time $S = \frac{dV_o}{dt}$	1 +	2	
2.	Symbol 	2	2	
3.	The rectifier circuit using op-amp is the precision rectifier. It is capable of rectifying signals of very small peaks (of the order of milli volt.). Also called small signal precision rectifier.	2	2	
4.	→ It is the range of frequencies over which the PLL can maintain lock with the incoming signal → Is usually expressed as percentage of the VCO frequency.	1 +	2	
5.	→ Is an electronic circuit to provide a predetermined d.c voltage → It generates a fixed output voltage of a preset magnitude that remains constant regardless of changes to its input voltage or load conditions.	1 +	2	
				10

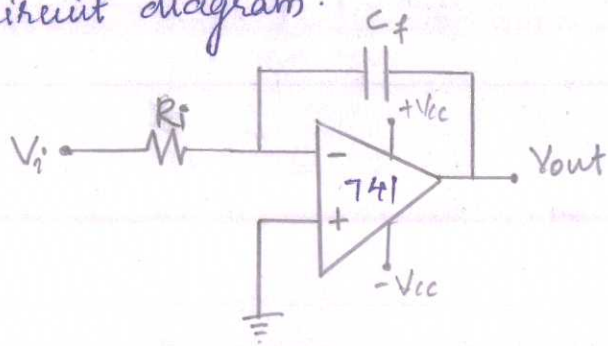


3. Circuit diagram.



→ output voltage is proportional to the time integral of the input voltage.

$$\rightarrow V_o = - \left[ \frac{1}{C_f R_i} \right] \int V_i dt.$$

4. Circuit diagram.

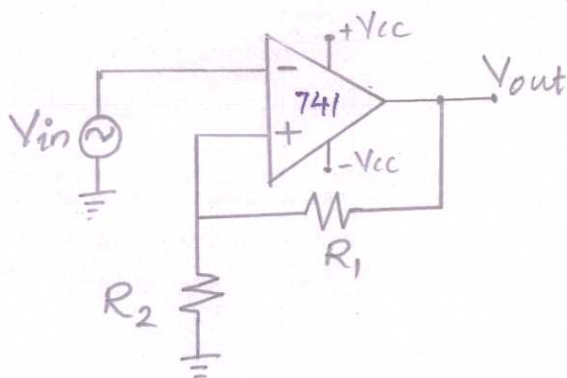

→ The comparator circuit with a positive feedback is the Schmitt trigger circuit.

→ Also called as regenerative comparator

→ It is used to avoid the unwanted triggering due to the noise in the basic comparator circuit.


→ output voltage is always at  $+V_{sat}$  or at  $-V_{sat}$

→ output voltage level is controlled by the feedback factor  $\beta = \frac{R_2}{R_1 + R_2}$


→  $+V_{ref} = +\beta V_{sat}$  → upper threshold voltage

$-V_{ref} = -\beta V_{sat}$  → lower threshold voltage

wave form

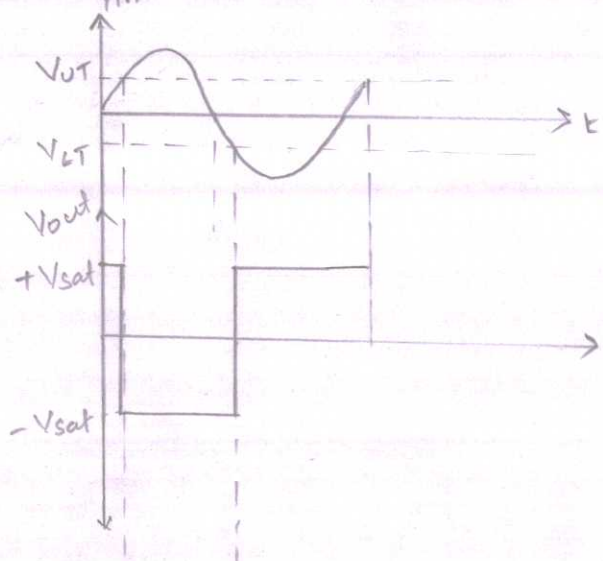


5.

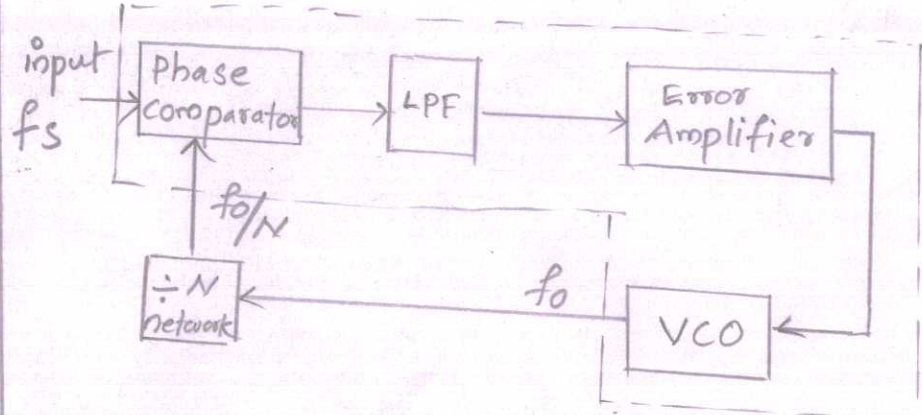


→ Since the output of the divider is locked to the input frequency  $f_s$  the VCO is actually running at a multiple of the input frequency  
 →  $f_o = N \cdot f_s$

6.

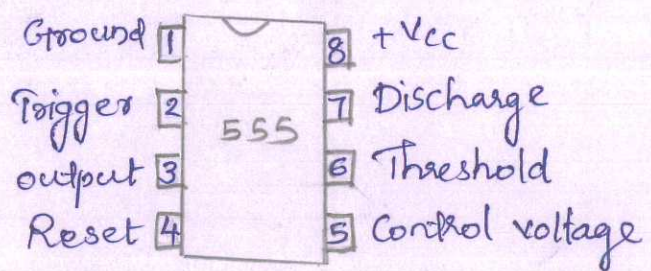

→ Functions of pins

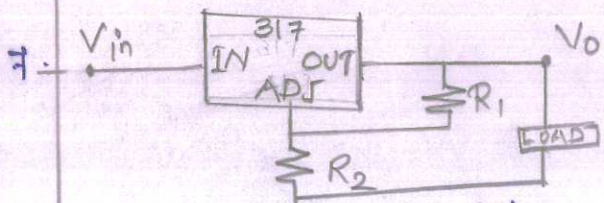

→ Adjustable regulator with three terminals  
 → Require two external Resistors

1 6

3

+ 6

3

2

+ 6

4

3

+ 6

3

30

III

PART - C

UNIT - I

(a) → CMRR :

Ratio of differential voltage gain to Common mode voltage gain 2

$$CMRR = 20 \log (A_d/A_{cm}) \text{ in dB}$$

→ Input offset voltage :

A small dc bias voltage applied between the input terminal to make the output zero Volt 2

→ input offset current :


Algebraic difference between the currents into the inverting and non-inverting terminals 2

$$I_{os} = |I_{B1} - I_{B2}|$$

→ Input bias current :

average of the currents entering into the inverting and non-inverting terminals of an op-amp.  $I_B = \frac{I_{B1} + I_{B2}}{2}$  2

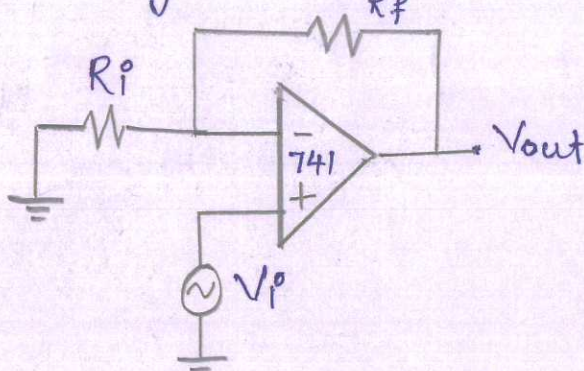(b) ekt diagram of Non-inverting amplifier.



→ Input is applied at (+)ve terminal  
 → outputs and inputs are in phase.

→ Voltage gain  $A_v = \left[ 1 + \frac{R_f}{R_i} \right]$  → 3

\* Derivation of equation

## OR UNIT- I

IV  
(a)

The popular packages are

1.) The metal can package (TO)

- available in 3, 5, 8, 10 and 12 leads
- chosen when heat dissipation is the main consideration.


2.) The dual in line (DIP) packages.

- for commercial applications.
- easy to use

3.) The flat package.


- Is a compact package.
- preferred for the circuit where space is critical.

→ diagram of each type

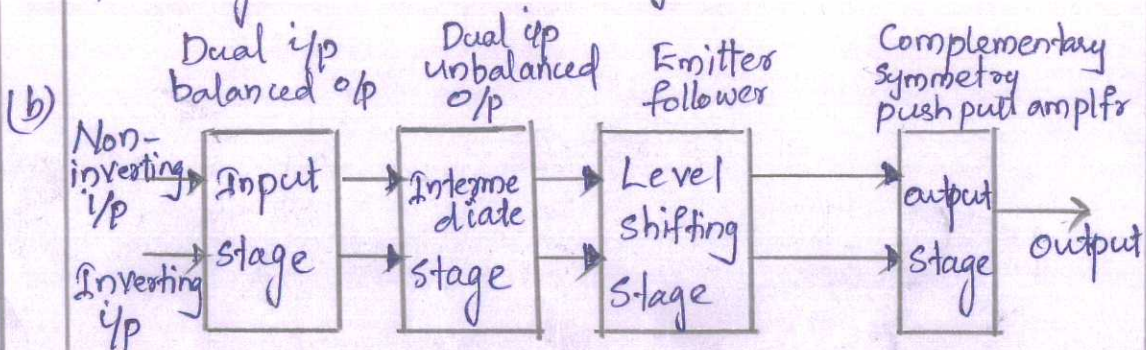

→ block diagram Explanation

V  
(a)

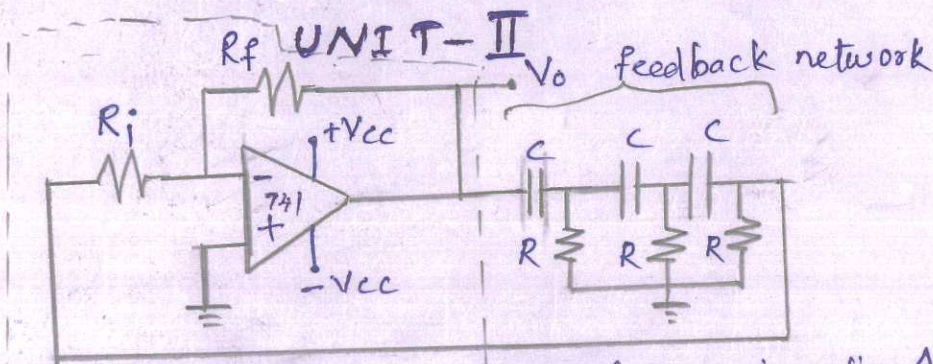


→ op-Amp as inverting Amplifier

→ Audio frequency Sine wave oscillator

→ frequency of oscillation  $f = \frac{1}{\sqrt{2} \pi R C \sqrt{6}}$

(b) Circuit diagram:

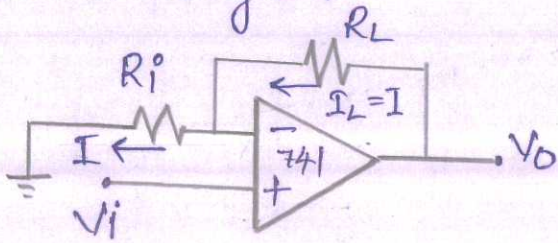


- A circuit that convert a voltage to a proportional current even though the load resistance may vary.
- For a single input the current in the load resistor  $R_L$  is given by  $I_L = I = V_i / R$

8

OR UNIT - II

VI (a)

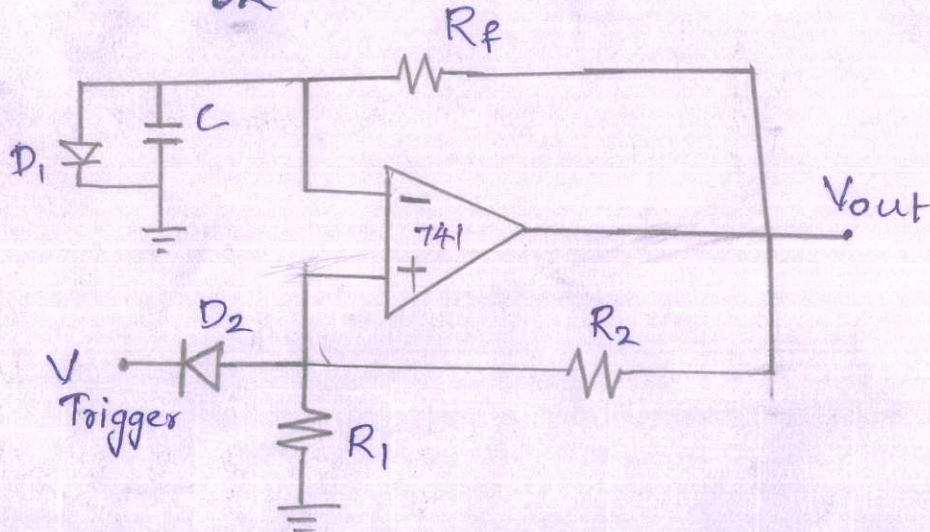

2 1/2


+

8

- wave form
- circuit explanation

→ 2  
+  
→ 3 1/2

(b)

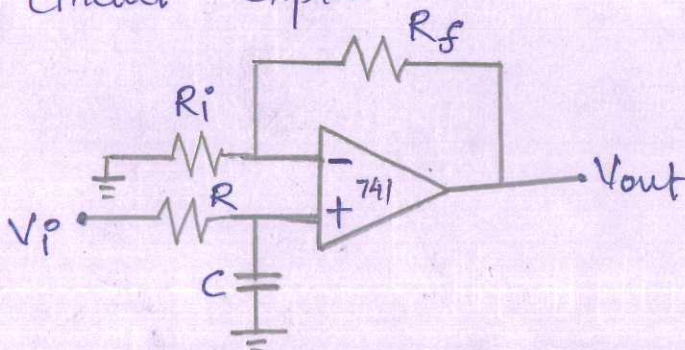

→ 2

+

7


- frequency response curve
  - circuit explanation
- gain of this filter  $A_F = [1 + R_f/R_i]$

→ 1 1/2  
+  
→ 3 1/2

# UNIT - III

VII  
(a)

PLL block diagram.

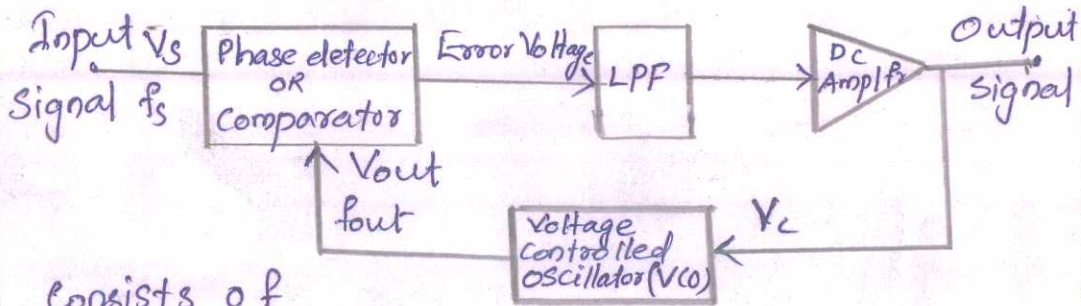

Consists of

- 1. Phase detector
- 2. Low pass filter
- 3. D.C amplifier
- 4. Voltage Controlled Oscillator VCO

explanation

3


+ 8

5

(b)

380 Audio power amplifier

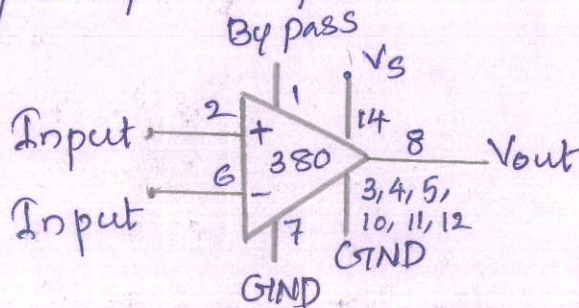- Much ideal for consumer applications.
- Require minimum number of external components.
- Internally fixed gain
- wide supply voltage range
- output is automatically self centering to 1/2 of the supply voltage.
- low quiescent power gain
- high peak current capability.
- low total harmonic distortion.
- high input impedance.




→ Input stage is a PNP-emitter follower

7

VIII

(a)


OR UNIT - III

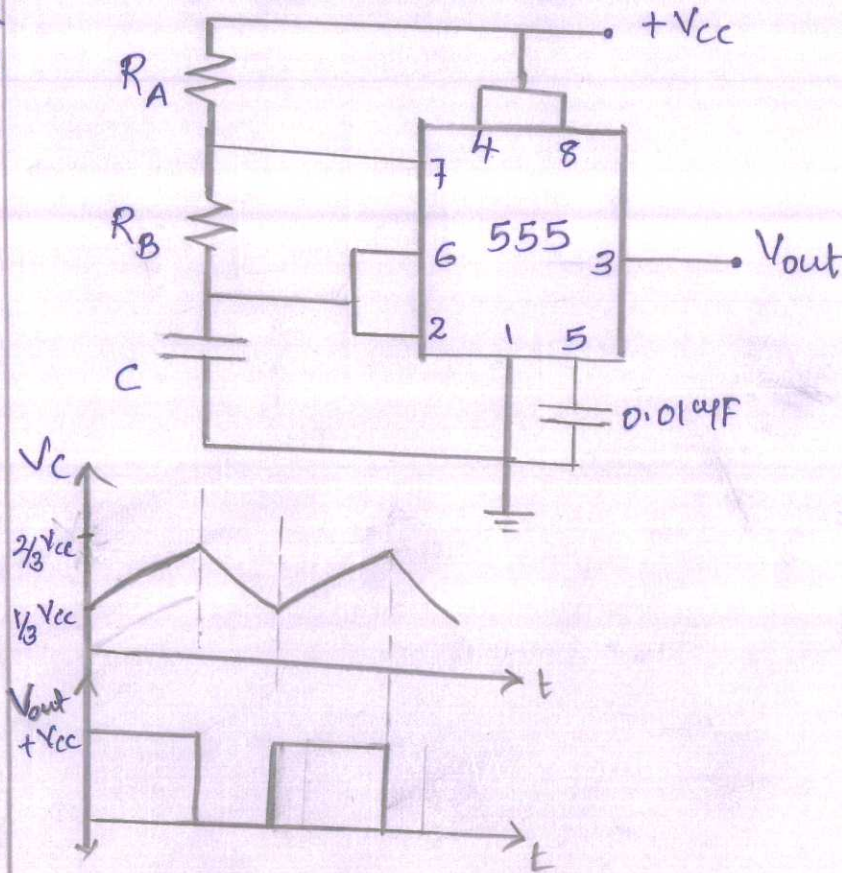

circuit explanation

- Astable multivibrator generate squarewave
- only two resistors and two capacitors are required to connect externally
- when internal transistor is cut off the external capacitor C charges through resistors and when the transistor ON, the capacitor discharges through  $R_B$  only. Thus the square wave is generated.


(b) Pin diagram

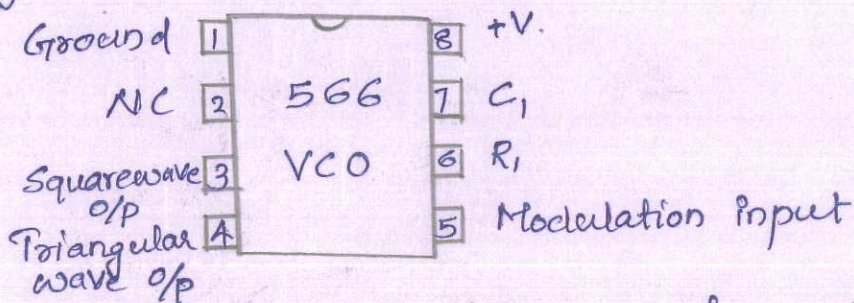

- In VCO frequency of oscillation can be controlled by externally applied voltage.
- VCO has 8 pins.
- pin <sup>function</sup> explanation

UNIT-IV

IX  
(a)

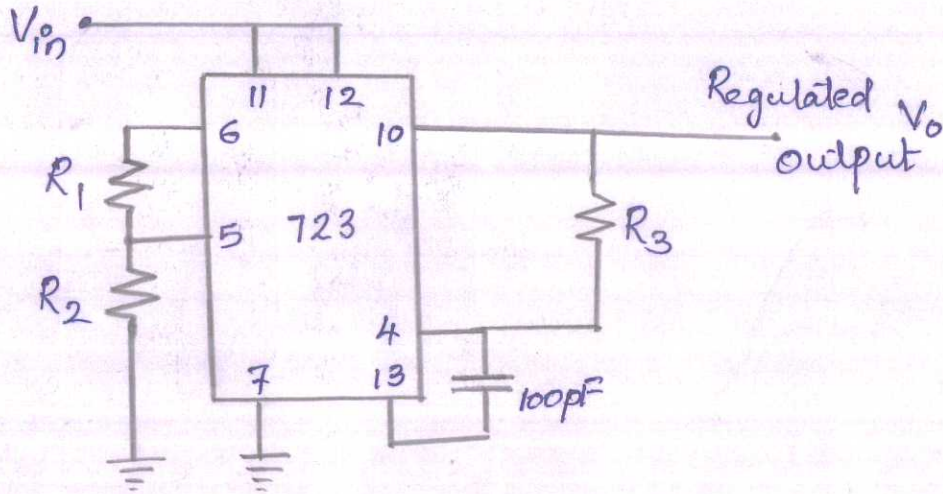

3 1/2

→ In the circuit of a low voltage regulator using 723 the output voltage will be regulated less than 7V

+ 8

→ pin 6 is the  $V_{ref}$  is connected to the pin 5 [  $V_{non-inv}$  ] through  $R_1$

→ output is feedback to the pin 4 (inverting pin) through  $R_3$


4 1/2

→ when output voltage becomes low, the voltage at the inverting terminal of 723 [error amplifier] also goes down, hence the output of error amplifier becomes more positive, then  $Q_1$  (transistor) in to more conduction.

→ opposite action takes place when the output voltage is increased.

$$V_{out} = V_{ref} \times \left[ \frac{R_2}{R_1 + R_2} \right]$$

(b)

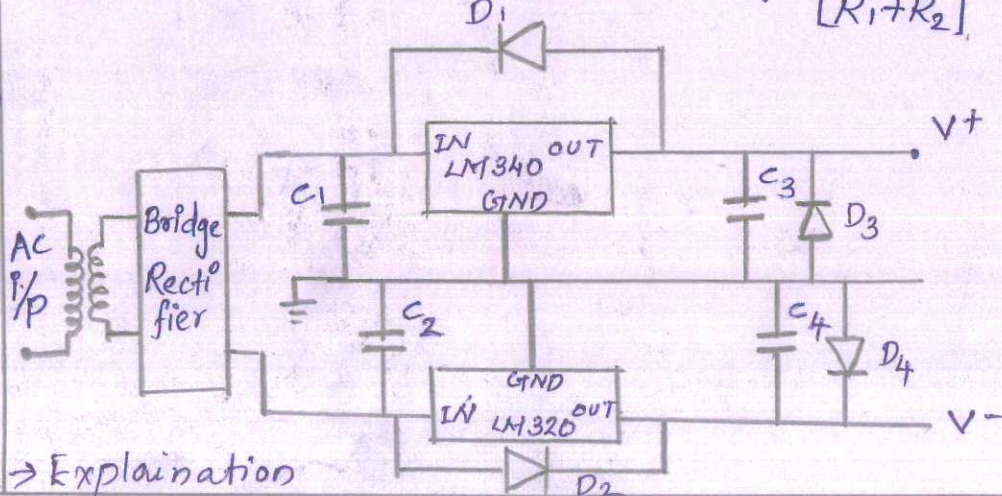

3 1/2

+ 7


3 1/2

→ Explanation

OR UNIT - IV

X  
(a)

Block diagram of SMPS

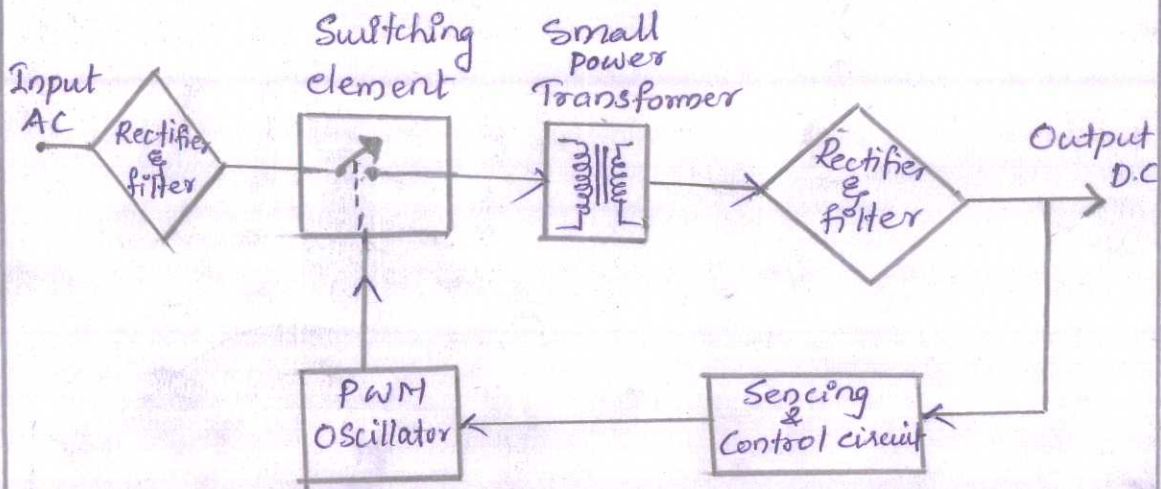


4

- overcome the shortcomings of linear voltage regulator
- used in most of the modern equipments
- Switching element is driven by PWM oscillator
- In SMPS, switching element is always operated in Switched Mode. i.e. either in cut off or in the saturation region.
- More efficient than linear
- dissipate very little power.
- Can operate at low ac ip.

8

4

(b)

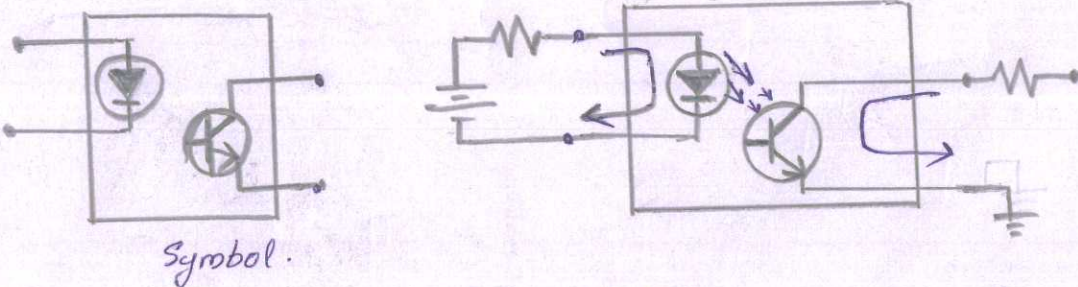

2

- Also known as opto Isolator.
- It consists of a photon emitting device (such as LED) whose flux is coupled through a transparent isolation materials (like air, glass, plastic) to some detectors (like, photo conductor, transistor.)
- applications → interface between sensors, coupling of signal between digital logic families, optical communication etc.

3

7

2

60