

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/
MANAGEMENT/COMMERCIAL PRACTICE, NOVEMBER - 2024**

DIGITAL ELECTRONICS

[Maximum Marks:75]

[Time: 3 Hours]

PART - A

I. Answer all the following questions in one word or one sentence. Each question carries 'one' marks.

(9 x 1 = 9 Marks)

Module Outcome Cognitive level

1	Binary equivalent of F_{16} is.....	M 1.01	U
2	Write 2's complement form of -35.	M 1.02	U
3	NAND and NOR areGates.	M 1.03	R
4	What is VLSI?	M 2.01	R
5	Draw the logic diagram of a half adder.	M 2.04	U
6	A flip-flop hasStable states.	M 3.02	U
7	Name asynchronous inputs in a flip-flop.	M 3.02	U
8	Asynchronous counters are also called.....	M4. 01	U
9	The.....Memory can store data even if power is turned off.	M4.04	U

PART - B

II. Answer any eight questions from the following. Each question carries 'Three' marks.

(8 x 3 = 24 Marks)

Module Outcome Cognitive level

1	Perform 2's complement addition. 1101-1001	M1.02	U
2	Show that $A \oplus B = A\bar{B} + \bar{A}B$ and construct the corresponding logic diagrams.	M1.03	U
3	Draw the logic diagram for $Y=(A + B)(A + \bar{B})(\bar{A} + \bar{B})$.	M1.04	A
4	Define the terms a) Fan-in b) noise margin	M2.02	U
5	Design a half subtractor using its truth table.	M2.04	A
6	Write the truth table and draw the logic diagram of 4 x 1 multiplexer.	M2.04	U

7	Differentiate between combinational and sequential logic circuits.	M3.01	U
8	Draw the logic diagram of a 4 bit Ring counter.	M3.04	U
9	Define modulus of the counter and write the number of states in a mod-4 counter.	M4.01	U
10	Compare RAM and ROM.	M4.04	U

PART - C

Answer all the questions from the following. Each question carries ‘seven’ marks.

(6 x 7 = 42 Marks)

Module Outcome Cognitive level

III.	Perform the following operations a) $69_{16} - 43_{16}$ b) $27_{16} - 73_{16}$ OR	M1.02	U
IV.	Reduce the expression $\sum m(1, 5, 6, 12, 13, 14) + d(2, 4)$ using K -map.	M1.04	A
V.	Realize EX-OR and AND gate using NOR gate. OR	M1.03	U
VI.	Minimize the following function using K- map and realize using logic gates. $F = \sum m(0, 1, 4, 5, 10, 11, 14, 15)$	M1.04	A
VII.	Design a 4 bit Gray to Binary code converter. OR	M2.04	U
VIII.	Design a 3 line to 8 line decoder.	M2.04	A
IX.	With the help of logic diagram explain the working of Serial in serial out shift register. OR	M3.03	U
X.	Explain Johnson counter with logic circuit.	M3.04	U
XI.	With the help of necessary diagrams explain the working of Parallel in Serial out shift register. OR	M3.03	U
XII.	Explain the working of JK flip flop with the help of a diagram using NAND gates.	M3.02	U
XIII.	Design a mod 6 asynchronous counter using T flip-flops. OR	M4.02	A
XIV.	Write notes on different types of RAM.	M4.04	U
