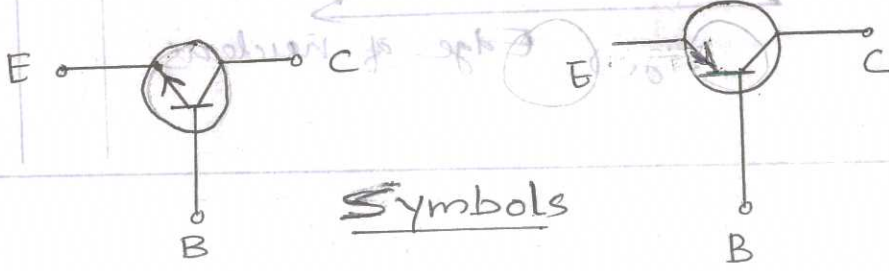


Revision: 15

Course code: (15) 2041

Course Title: BASIC ELECTRONICS


Qst. No	Scoring Indicators	Split up score	Sub Total	Total
1.	Power supply Impedance matching Isolate two circuits electrically	2		
2.	Value of inductance Current rating Tolerance Temperature coefficient Stability d.c. resistance Q-factor Frequency range	2		
3.	Diffusion current in semiconductor is the current which flows as a result of a gradient of carrier concentration (Due to the difference of carrier concentration from one region to another).	2		
4.	Shunt Capacitor Filter Series Inductor Filter Choke Input L.C. Filter π -Filter	2		
5.	<p align="center"> <u>NPN Transistor</u> <u>PNP Transistor</u> </p>  <p align="center"><u>Symbols</u></p>	2		
		5x2 = 10		10

Qst No:	Scoring Indicators	split up score	Sub Total	Total
	PART-B			

1. Value of Capacitance
 Working Voltage
 Tolerance
 Stability
 Leakage current
 Temperature Coefficient

6x1 = 6	6
---------	---

2. Band Energy

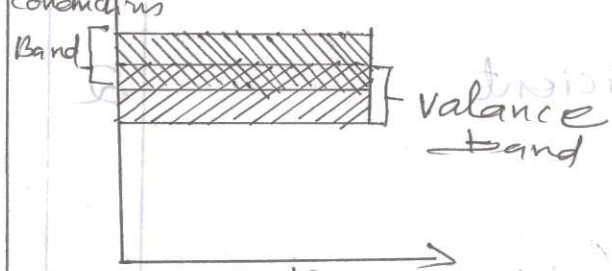

Semi Conductor

Fig (a)

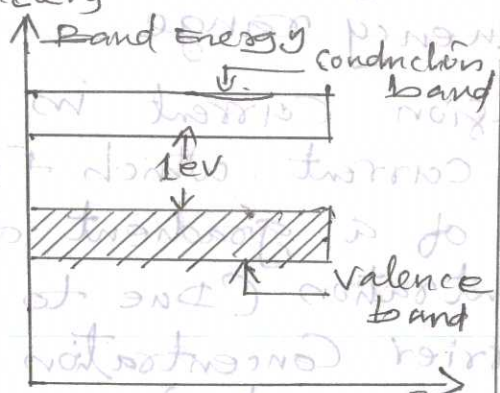


Fig (b)

Insulator


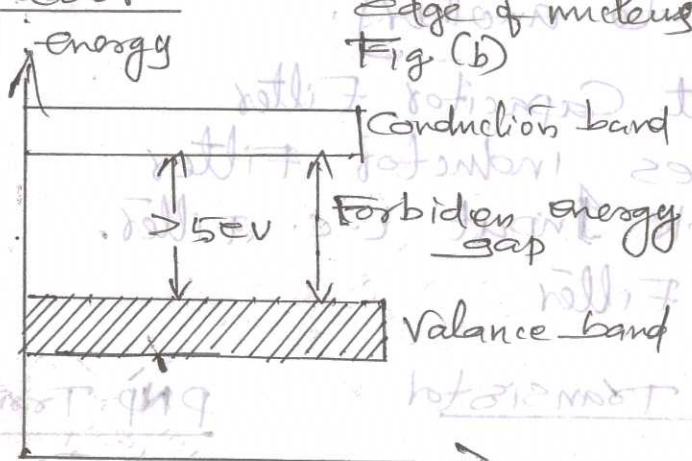


Fig (c)

1	1	3	6
1	1	3	6

Qst. No.	Scoring Indicator	split score	sub score	Total
----------	-------------------	-------------	-----------	-------

3.

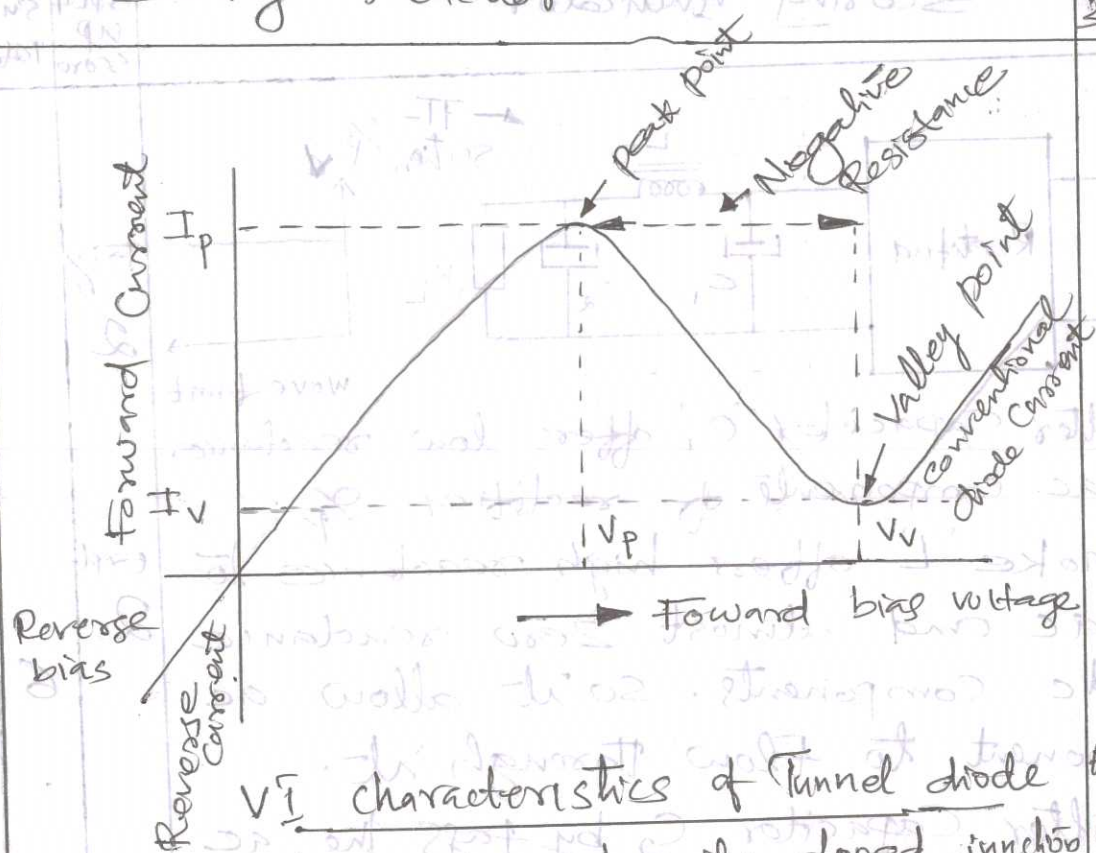


VI characteristics of Tunnel diode Fig 3+

Tunnel diode is a heavily doped junction diode. It has a negative resistance region at low forward bias. It works on the principle of tunneling which is obtained by creating an extremely thin depletion layer. It is also called ESAKI diode. The width of the junction barriers varies inversely as the square root of the impurity concentration. For such thin potential energy barriers, the electrons will penetrate through the junction rather than surrounding them. This quantum mechanical behavior is referred to as tunneling and hence these high impurity density PN junction device are called tunnel diodes.

Fig 3+
Exp 6
3

Scoring Indicator

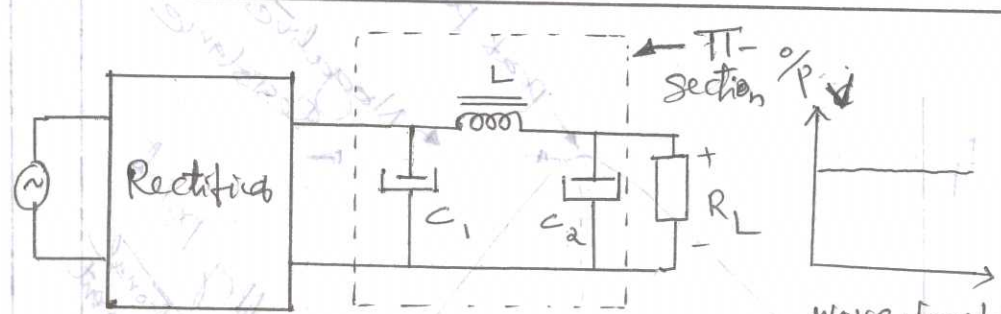Qst. No		Split UP Score	Sub Total	Total
4.	 <p>① Filter Capacitor C_1 offers low reactance to ac components of rectified $\%p$.</p> <p>② choke L offers high reactance to the ac and almost zero reactance to dc components. so it allow dc Component to flow through it.</p> <p>③ Filter Capacitor C_2 by tags the ac Component which the choke has failed to block. So pure dc appears across R_L</p> <p><u>advantages:</u></p> <ol style="list-style-type: none"> 1. Ripple less output. 2. More output voltage. 3. Suitable to be used with both half wave and Full wave Rectifier 	2 2 6 2		
5.	<p>TUF is defined as the ratio of d.c. Output power to a.c. power supplied to it by the Secondary winding.</p> <p>i.e, $TUF = \frac{P_{dc}}{P_{ac}} \text{ (rated)}$</p> <p>The ratio of r.m.s Value of a.c Component to the d.c. Component in the rectifier output is known as ripple factor</p> <p>i.e, Ripple factor = $\frac{\text{r.m.s. Value of a.c Component}}{\text{Value of d.c. Component}}$</p> <p>$= \frac{I_{ac}}{I_{dc}}$</p>	2 6 2		

Qst. No.:

Scoring indicators

Split's up score Total Total

The ratio of d.c. power output to the applied input a.c. power is known as rectifier efficiency.
 i.e., Rectifier efficiency, $\eta = \frac{\text{d.c. power } \%}{\text{Input ac power}}$

2

6.

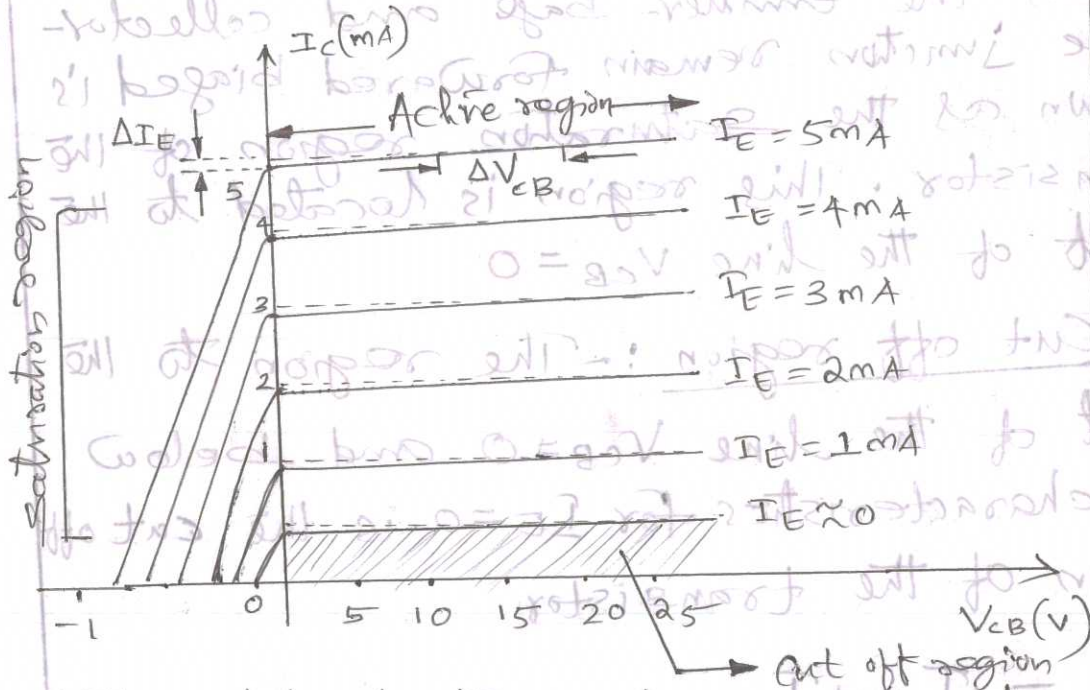


Fig 2
2

The plot of the collector current I_C as a function of the collector to base voltage V_{CB} with the emitter current I_E as a parameter is referred to as CB output characteristics

The output characteristics can be divided into three distinct regions

- * Active region
- * Saturation region
- * Cut off region

Req:

1

Qst No

Scoring Indicators

SPL/ Sub
Up
Score Total

(i) Active region :- This is the Normal operating region of a transistor when used as amplifier. In this region the emitter junction will be in forward bias and collector junction will be in reverse bias.

(ii) Saturation region :- The region, where both the emitter-base and collector-base junction remain forward biased is known as the saturation region of the transistor. This region is located to the left of the line $V_{CB} = 0$

(iii) Cut off region :- The region to the right of the line $V_{CB} = 0$ and below the characteristic for $I_E = 0$ is the cut off region of the transistor.

7

$$I_E = I_B + I_C \quad \text{--- (1)}$$

Since $\frac{I_C}{I_B} = \beta$ $\frac{I_C}{I_E} = \alpha$

add Δ in --- (1)

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\therefore \beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} \quad \text{divide by } \Delta I_E$$

Qst No

Scoring Indicators

SPUT UP Score

Sub Total

$$\beta = \frac{\Delta I_C}{\Delta I_E} = \frac{\alpha}{1-\alpha}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\beta(1-\alpha) = \alpha$$

$$\beta - \alpha\beta = \alpha$$

$$\beta = \alpha + \alpha\beta = \alpha(1+\beta)$$

$$\alpha = \frac{\beta}{1+\beta}$$

PART - C Unit - I

Areas of Application of electronics:-

- ① Entertainment & Communication List 3 mark
 - ② Defence Application
 - ③ Industrial Application 7
 - ④ Medical Science EXPT: 4 mark
 - ⑤ Instrumentation Type 3 mark
- ⑥
1. Potentiometer
 2. Rheostat
 3. Preset

Scoring Indicators

Split up	Score	Total

Applications of Variable Resistors

① Potentiometer :- Used in circuits with smaller power demand such as volume control in audio equipments, brightness and contrast control in TV, preset potentiometer in measuring instruments.

② wire wound Resistor :- As potential divider in several equipment, such as balance controller, small motor controller, servo controller, television receiver, analog computers.

③ Rheostat :- To control voltage and current in AC and DC circuits such as temperature control, welding control, light dimmer, motor speed control.

IV/a

→ It is an electrochemical double layer capacitor (EDLC)

→ It has an unusually high energy density

→ It stores energy electrostatically by polarizing an electrolytic solution

→ No chemical reactions involved in its energy storage mechanism

→ This mechanism is highly reversible allowing the ultra capacitor to be charged and discharged million of times

Expt.

5 8

Expt.

5mk

d

Qst No

Scoring indicators

Split up Base

Total

Advantages

- a) long life
- b) Good reversibility
- c) Very high rates of charge and discharge
- d) Extremely low internal resistance
- e) High output power
- f) improved safety
- g) Rapid charging
- h) Simple charging methods

4 points

4 mark

9 mark

- 1) Iron Core inductors
- 2) Ferrite Core inductors
- 3) powder core inductor
- 4) Air core inductor

4 points

4 mark

Applications

- Filtering the ripples in Power Supplies 2 points
- AF choke to block AF signal in various circuits 2 mark
- RF choke provide high impedance to RF

6

12/22

Roll No

Scoring Indicators

Split up Score Total

V/a

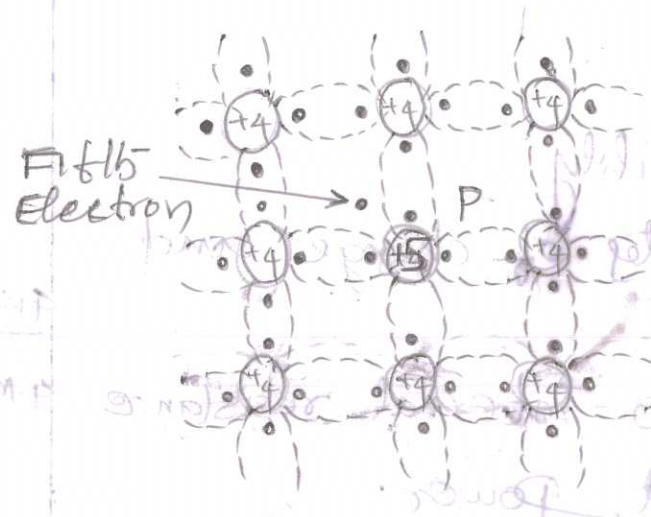


Fig: 5 mark

N-type Semiconductor is an extrinsic semiconductor doped with a pentavalent impurity like, Antimony, phosphorus, Arsenic etc.

Figure shows the crystal structure obtained when a silicon is doped with a pentavalent impurity. Here four of the five valence electrons of impurity atom form covalent bonds with the surrounding four silicon atoms and the fifth will be nominally unbounded and is free to move about the crystal. This electron can be easily excited from the valence band to the conduction band by applying negligible amount of energy.

Expts 4 mark

Scoring Indicators

SPLIT UP Score Total

Qst No

b.

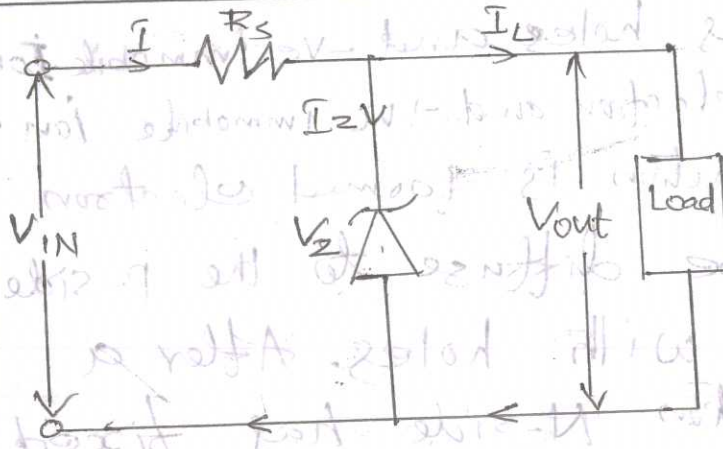


Fig. 3

Zener diode as voltage Regulator

A Zener diode, when working in the break down region, can serve as a voltage regulator. In Fig. V_{IN} is the input d.c. voltage whose variations are to be regulated. The Zener diode is reverse connected across V_{IN} . When p.d. across the diode is greater than V_Z it conducts and draws relatively large current through the series resistance R_S . The load resistance R_L across which a constant voltage V_{out} .

6 mark

Exp: 3

VI a.

When a p-type semiconductor is suitably joined with n-type semiconductor PN junction is formed.

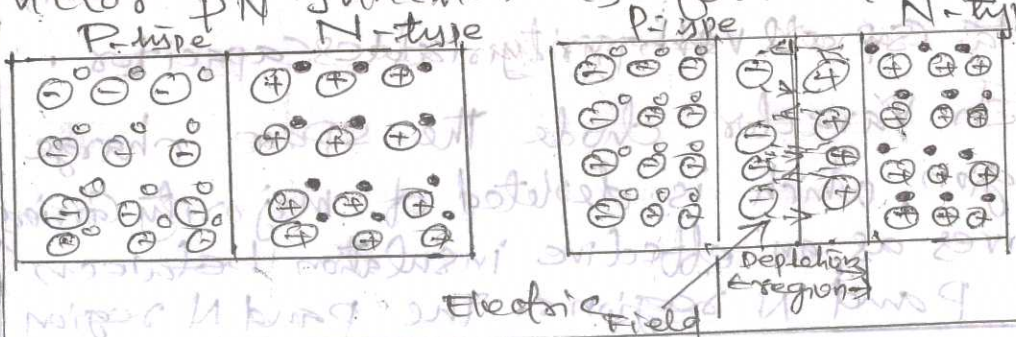


Fig 5 mark

Qst No	Scoring Indicators	SPLN up Score
--------	--------------------	---------------

P-region has holes and -ve immobile ion. N-region has electron and +ve immobile ion. when pn junction is formed electron in the N-type diffuse to the p-side and combine with holes. After a few recombination N-side has fixed +ve charges and p-side fixed -ve charges. Thus a barrier is set up which prevents further movement of charge carriers. This region is called depletion region or space charge region.

VI/b.

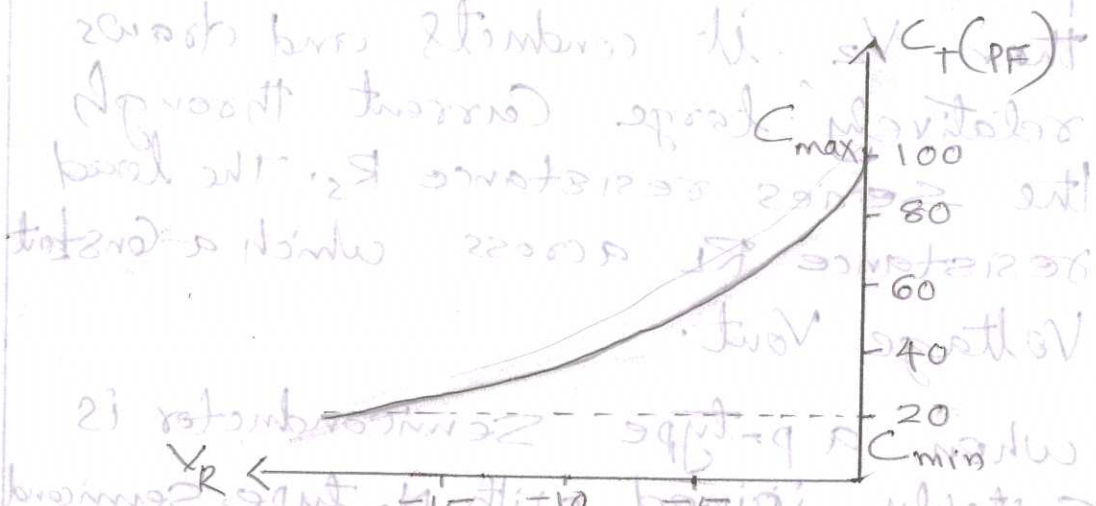


Fig 2-

Varactor diode is also called Varicap, Volta Cap. or voltage variable capacitor.

In Varactor diode the space charge region, which is depleted of majority carriers serves as an effective insulation between the p and n regions. The p and n region

Qst No

Scoring Indicators

SPMT
MD
Score

act as the plate of the Capacitor while the space-charge region act as the insulating dielectric.

Fig shows the Variation of Capacitance in a varactor diode with reverse bias Voltage. It indicates that the Capacitance decreases with increase in reverse bias, this is because of the increase in the width of the depletion layer and hence the distance between the plates.

The Capacitance offered by PN junction is given by the relation

$$C = \epsilon A / W$$

where,

- C is the Capacitance
- A is the area of junction
- W is the width of depletion region

EXP: 4 6

VII
a

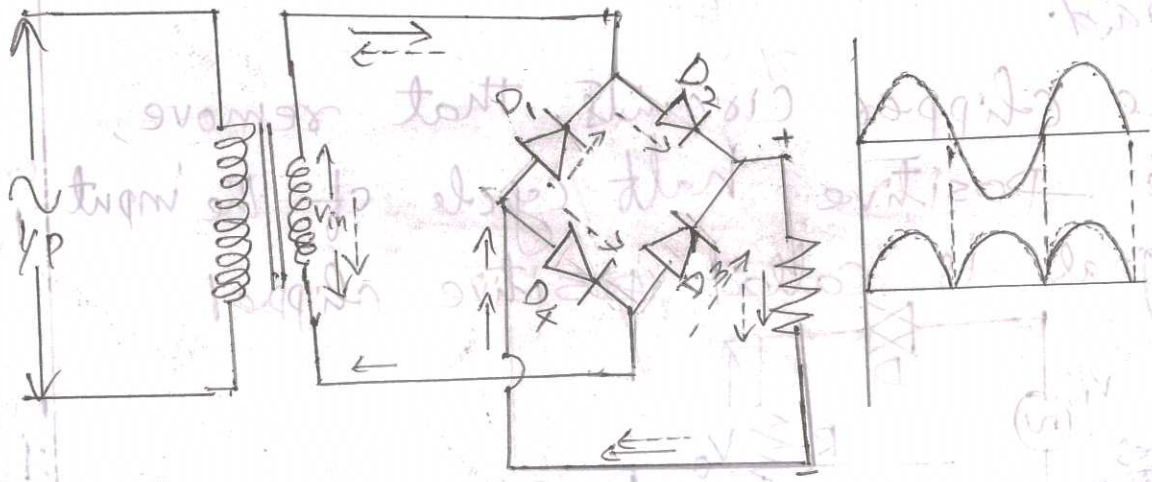



Diagram 4 Mark
Exp: 3 Mark
1 phase 2 Mark

Scoring Indicators

SPLIT UP Total Score

During the +ve half cycle of the secondary voltage, diodes D_2 and D_4 are conducting and diodes D_1 and D_3 are non conducting. Therefore current flows through the secondary winding, diode D_2 , load resistor R_L and diode D_4 as shown in fig. During -ve half-cycles of the secondary voltage, diodes D_1 and D_3 conduct, and the diodes D_2 and D_4 do not conduct. The current therefore flows through the secondary winding, diode D_1 , load resistor R_L and diode D_3 . In both cases, the current passes through the load resistor in the same direction. Therefore, a fluctuating unidirectional voltage is developed across the load.

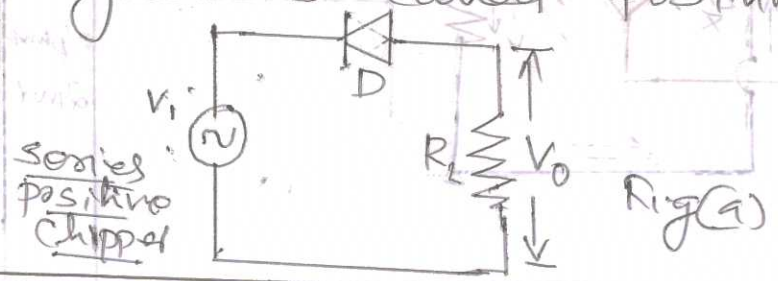VII/b) The clipper circuits that remove the positive half cycle of the input signal is called positive clipper



Qst No


Scoring Indicators

Series positive Clipper


During the positive half cycle of the input signal the diode doesn't conduct and act as an open circuit. Hence the positive half cycle of the input signal doesn't appear at the output. During -ve half cycle of the input voltage the diode conducts and act as a short circuit. Thus only -ve half cycle will appear at the output as shown in fig (c).

Fig 3
3
3

6

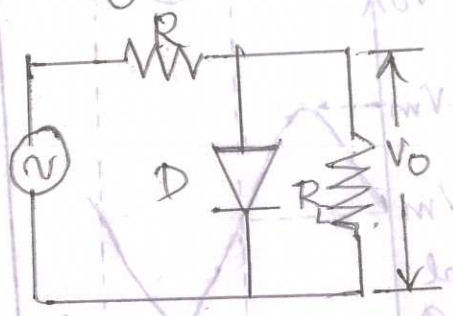

Shunt positive Clipper

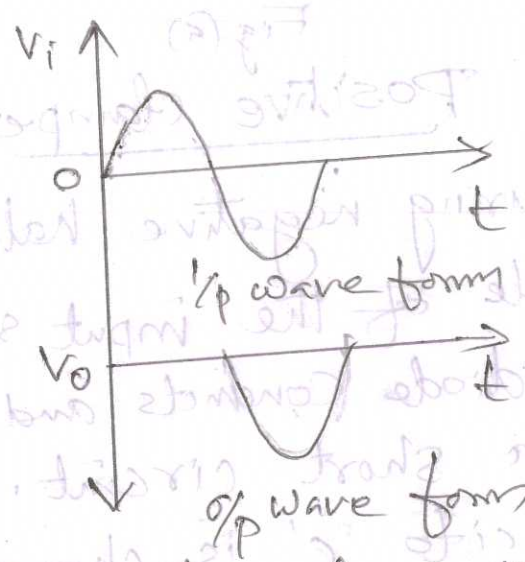

During positive half cycle of the input signal the diode conducts and acts as a short circuit. Hence there will be no voltage drop across diode. During -ve half cycle of the input voltage, the diode doesn't


Scoring Indicators

SPLIT UP SCORE	TOTAL
----------------	-------

Conduct and act as an open circuit. Thus the -ve half cycle of the input voltage appears at the output as shown in fig(c).



VIII
a)

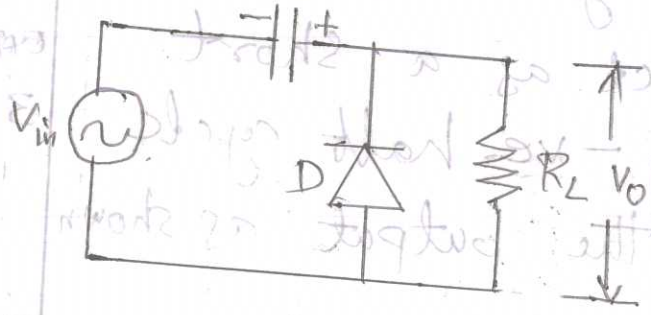clamping circuits simply clamp (ie shift up or down) the input signal to different d.c. level.



Fig(a)

Positive clamper

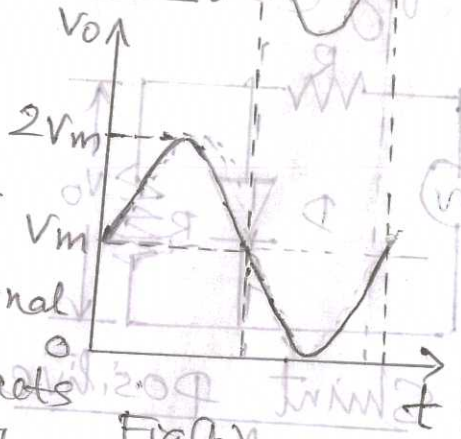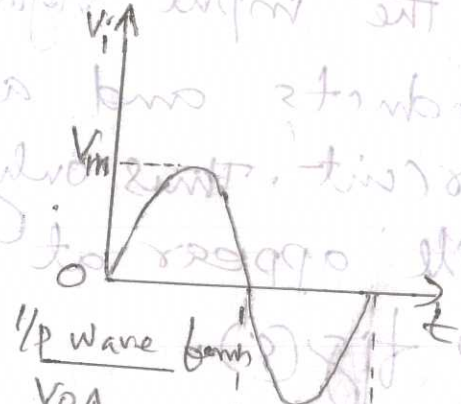

Fig(b)
o/p. wave form

During negative half cycle of the input signal the diode conducts and acts as a short circuit. The capacitor 'c' is charged to V_m at the peak -ve of the input signal with the polarity as marked.

During +ve half cycle of the input signal capacitor acts like a battery of V_m volts, which adds to the

Prqs
2 marks

Wave form
2

9

Ex: 5

Qst No.

Scoring Indicators

SPUR
mp
Score

Total

positive half cycle. During +ve half cycle of the input signal, the diode is reverse biased and acts as an open circuit.

The output voltage across the load resistor R_L will be =

$$V_m + V_m = 2V_m$$

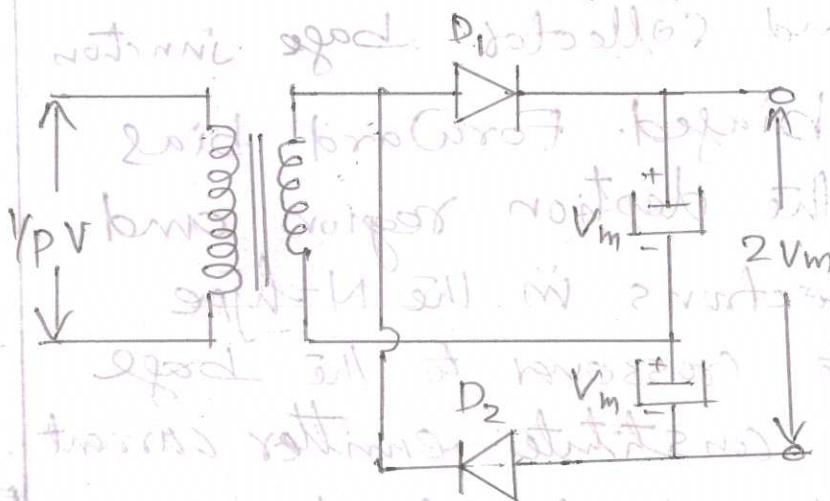


Fig 3 mark

During the positive half cycle of the secondary voltage diode D_1 conducts charging the capacitor C_1 to the peak voltage V_m . At this time diode D_2 is non conducting.

During -ve half cycle diode D_2 conducts, charging the capacitor C_2 to V_m with polarity marked while diode D_1 is non conducting. Since both capacitor C_1 and C_2 in series, the final output voltage is approximately $2V_m$.

6 mark

Expt: 3

VIII
b

Scoring Andicators

dist No

SPLIT UP Total Score

IX a

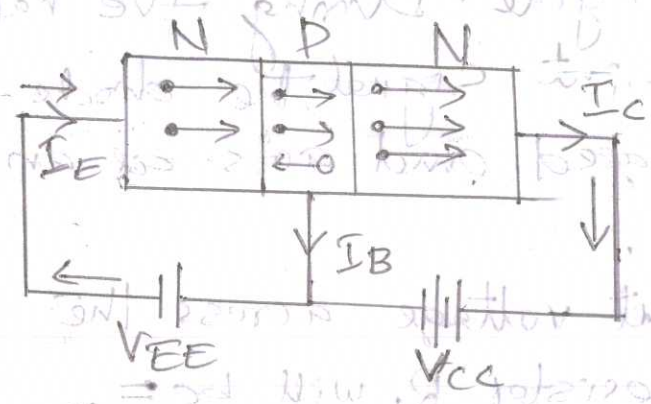


Fig 3

Emitter base junction is forward biased and collector base junction reverse biased. Forward bias reduces the depletion region and causes electrons in the N-type emitter to crossover to the base region to constitute emitter current I_E . As base is lightly doped and thin, no of holes in the base is very small. Few electrons combine with holes at the base and constitute the base current I_B . When collector is reverse biased, the injected majority carrier will appear as minority carriers. To the minority carriers reverse bias appears as forward bias and easily cross to the collector region to constitute collector current I_C .

11111
d
6

expl

3

Scoring Indicators

SPLIT UP SCORE TOTAL

Qst No
IX
b

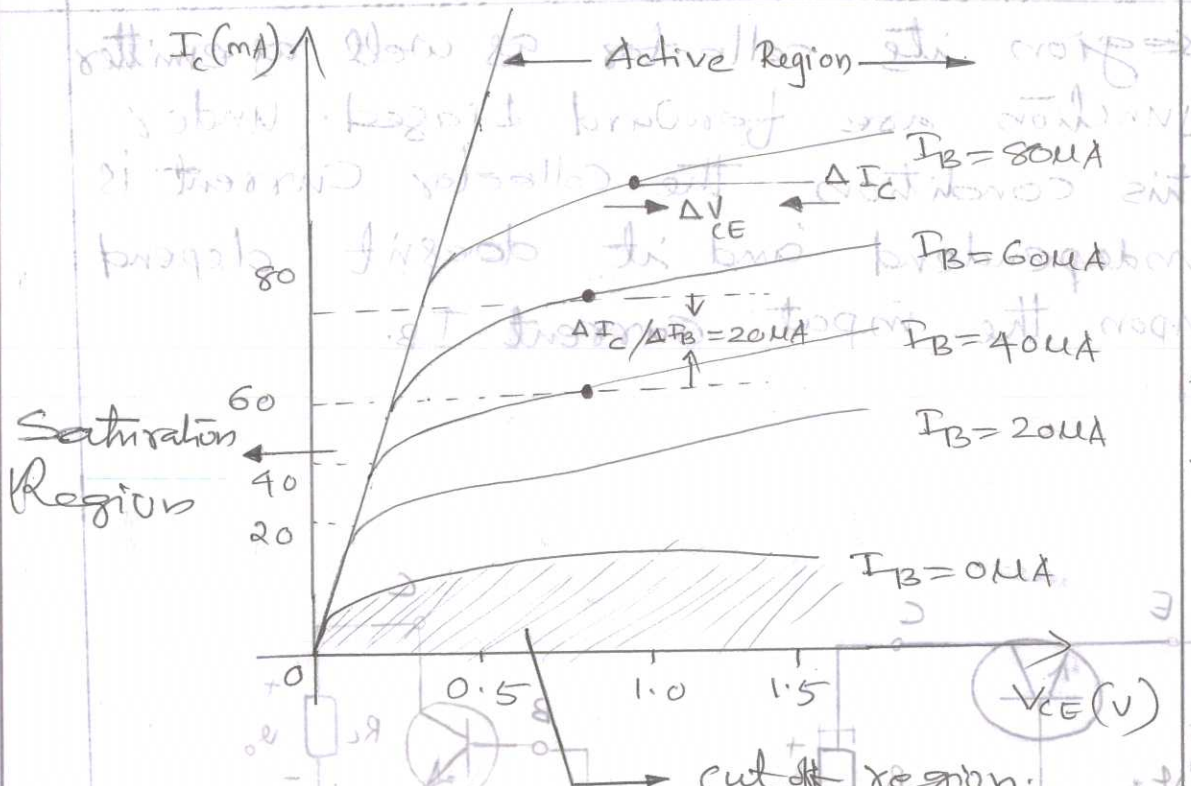


Fig 4-

Here collector current I_c is plotted against the collector to emitter voltage V_{ce} with base current I_b as parameter.

Active Region

In this region the emitter junction is in forward bias state and collector junction is in reverse bias. In the fig, the active region is above the curve for $I_b = 0$.

Cut off region

In this region both junctions of the transistor are reverse biased. It is the region to the right of the line $V_{ce} = 0$ and below the curve $I_b = 0$.

Saturation region

When a transistor operates in this

9

EXP 5


Qst No

Scoring Indicators

SPLIT UP SCORE


region its collector as well as emitter junction are forward biased. Under this condition, the collector current is independent and it doesn't depend upon the input current I_B .

$\frac{X}{a}$

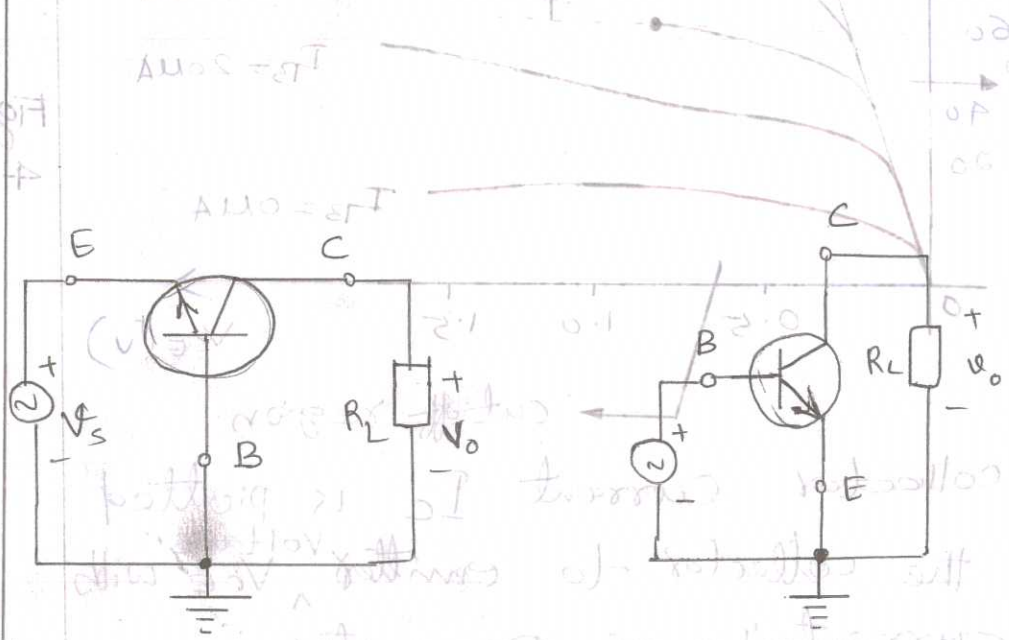

Common - Base Configuration (CB)

Common-Emitter Configuration

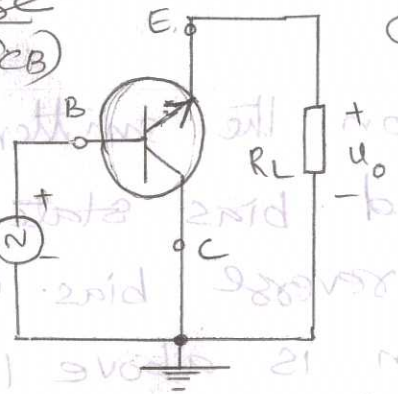

Common - collector Configuration

Qst. No

Scoring Indicators

SPLIT UP Score

Comparison of Transistor Configuration.

Characteristics	CB	CE	CC
* r_p resistance	Low (100-2)	Moderate (750-2)	High (750K-2)
* r_o resistance	High (500K-2)	Moderate (45K-2)	Low (50-2)
* current gain	< 1 (0.98)	High (400)	High (400)
* Voltage gain	About 150	About 500	< 1
* Leakage Current	Less (5MA for Ge and 1MA for Si)	More (500MA for Ge and 20MA for Si)	More (500MA for Ge and 20MA for Si)
* Application	HF circuit	AF circuit	For impedance matching

Comp: 6 9

X
b

The input resistance of a Transistor can be found from the slope of the input characteristic curve. Here the dynamic input resistance is the ratio of change in emitter base voltage to the resulting change in emitter current at constant collector-base voltage.

$$i.e. r_i = \frac{\Delta V_{EB}}{\Delta I_E} \Big|_{V_{CB} \text{ constant}}$$

The typical value of input dynamic resistance falls within 20 ohms to 100 ohms

The dynamic output resistance is the ratio of change in collector to base voltage to the corresponding change in collector current at constant emitter current

$$i.e. r_o = \frac{\Delta V_{CB}}{\Delta I_C} \Big|_{I_E \text{ constant}}$$

6

Q.21
No

Scoring Indicators

Split
up
Score

Total

Since the output characteristics curve are very flat, change in collector current correspondingly to the change in collector-base voltage is very little. Therefore the output resistance of CB configuration is very high of the order of mega ohms.

The input resistance of a transistor can be found from the slope of the input characteristic curve. Here the dynamic input resistance is the ratio of change in emitter base voltage to the resulting change in emitter current at constant collector-base voltage.

$$r_{ie} = \frac{\Delta V_{EB}}{\Delta I_E} \quad | \quad V_{CB} \text{ constant}$$

The typical value of input dynamic resistance falls within 20 ohms to 100 ohms. The dynamic output resistance is the ratio of change in collector base voltage to the corresponding change in collector current at constant emitter current.

$$r_{oc} = \frac{\Delta V_{CB}}{\Delta I_C} \quad | \quad I_E \text{ constant}$$