

TED (15) 3133
(Revision-2015)

N20-00887

Reg.No.....
Signature.....

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/
MANAGEMENT/COMMERCIAL PRACTICE, NOVEMBER-2020

DIGITAL COMPUTER PRINCIPLES

[Maximum marks: 75]

(Time: 2.15 Hours)

PART – A

(Answer any *three* questions in one or two sentences. Each question carries 2 marks)

- I. (1). Define base or radix of a number system.
(2). Write the number of cells or squares in an n-variable K-map.
(3). List basic types of shift registers.
(4). Define resolution of DAC.
(5). Write the number of address inputs in a 32x4 memory. (3 x 2 = 6)

PART – B

(Answer any *four* of the following questions. Each question carries 6 marks)

- II. (1). Define BCD code. Express the decimal number 653 in BCD and XS-3 code.
(2). Prove that $AB + A'C + BC = AB + A'C$
(3). Define minterm. Expand $A'+B'$ to minterms.
(4). Write the truth table and logic expression for octal to binary encoder.
(5). Show how a J-K flip-flop can be converted to a T flip-flop.
(6). Design a 4 bit Ring counter using D flip-flop.
(7). Write any three comparison between PAL and PLA. (4 x 6 = 24)

PART – C

(Answer *any of the three units* from the following. Each question carries 15 marks)

UNIT – I

- III. (a). Convert the hexadecimal number 4F7.A8 to Decimal, Octal and Binary. (9)
(b). Explain with an example the procedure for converting a binary code to a Gray code. (6)

OR

- IV. (a). Show how an OR gate is implemented by NAND gate and NOR gate. (8)
(b). Convert the binary number 1111001.1101 to Hexadecimal and Octal. (7)

UNIT-II

- V. (a). Define k-map. Obtain the minimal SOP expression for $\sum m(2,3,5,7,9,11,12,13,14,15)$ (8)
(b). Draw a logic circuit for half adder and explain its operation. (7)

OR

- VI. (a). Draw the block diagram for 4 bit parallel binary adder and explain its operation. (8)
(b). Draw the logic circuit for a 2 input multiplexer and explain its operation. (7)

UNIT-III

- VII. (a). Define flipflop. Explain the operation of D-flip flop with truth table and logic diagram. (8)
(b). Explain the operation of a 4-bit Serial –in Serial –out shift register with proper diagram. (7)

OR

- VIII. (a). Define counter. Differentiate between synchronous and asynchronous counters. (8)
(b). Design a mode-6 asynchronous counter. (7)

UNIT-IV

- IX. (a). Define DAC. Draw the block diagram of a 4-bit DAC and explain the operation. (8)
(b). Define Accuracy, Settling time and Monotonicity of DAC. (7)

OR

- X. (a). Define ADC. With logic diagram, explain the operation of an ADC. (8)
(b). Define ROM. Compare PROM and EPROM. (7)