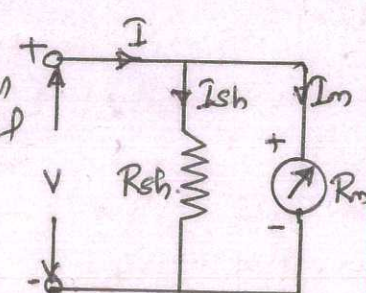




Scheme of Valuation  
(Scoring Indicators)

Revision - 2015 Course Code - 4041  
 Course Title - Electronics Instruments And Measurements

Qst No.	Scoring Indicators	Split up Score	Sub Total	Total
<u>PART - A</u>				
I.1.	It is the closeness or nearness to which an instrument can read the true or actual value of the quantity or variable being measured	2	2	
2.	a) Measurement of voltage and current b) Measurement of phase, Power and Power factor	1+1	2	
3.	When a number of thermocouples are connected in series it is called a thermopile.	2	2	
4.	a) Measurement of signal purity (b) Modulation characteristics (c) pulse shape analysis (d) Noise measurement	1x2	2.	
5.	A system in which the controlling action or input is somehow dependent on the output or change in output is called a closed loop system.	2	2	
<u>PART - B</u>				
II.1.	<u>Advantages</u> :- The input impedance is high; frequency range is high; Simple circuit; Cost is less; Construction is rugged; It is less suffered from electric noise <u>Disadvantages</u> :- Accuracy is less; resolution is poor; Not Compact in size; reliability and repeatability are poor.	3+3	6	
2.	The basic movement of a d.c. ammeter is a PMMC galvanometer. The coil winding of a basic movement is small and light, it can carry only very small currents when large currents are to be measured, it is necessary to bypass a major part of the current through a resistance called a shunt resistor as shown in fig. The resistance of shunt can be calculated using conventional circuit analysis.		2+4 =6	6

Where,  $R_{sh}$  = resistance of the shunt;  $R_m$  = internal resistance of the movement;  $I_m$  = full scale deflection current of the movement;  $I_{sh}$  = Shunt current  
 $I$  = Total current


Since the resistance is in parallel with the meter movement, the voltage must be the shunt and the movement must be same

$$\therefore V_m = V_{sh} \quad \therefore I_m R_m = I_{sh} R_{sh}$$

$$\therefore R_{sh} = \frac{I_m R_m}{I_{sh}} \quad \text{or, } I_{sh} = I - I_m$$

$$\therefore R_{sh} = \frac{I_m R_m}{I - I_m}$$

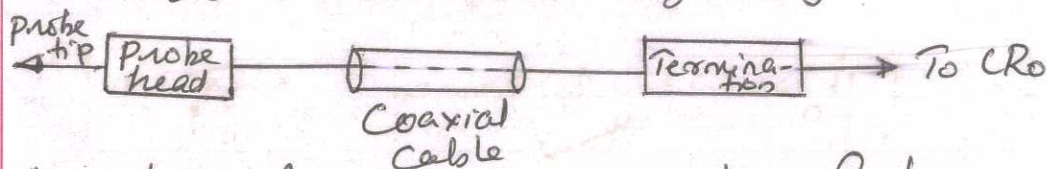3. A probe is a conductor used to establish a connection between the circuit under test and the measuring instrument. While connecting the test circuit the probe does not alter, load or disturb the circuit and signal conditions to be analysed. The probe should have high impedance, the probe bandwidth should be as high as possible.



Many types of probes can be classified below.

- (1) Direct probe (2) Isolation probe (3) High impedance or 10:1 probe (4) Active probe (5) Current probe (6) Differential probes etc...

Direct probe:- The simplest types of probe are the test lead. Test leads are simply convenient lengths of wire connecting the CRO input to the point of observation. At the end of CRO, they usually terminate with lugs, banana tips or other tips to fit input jacks of the scope, and at the other end has a crocodile clip or any other convenient means for connection to the electronic circuit.

Isolation probe:- The input capacitance of the scope and the stray capacitance of the test lead are very high. It causes the sensitive to break into osci

Page  
1  
15-1  
Page-4

1+1+4  
=6

6

lation when CRO connected. This effect can be prevented by an isolation probe.

High impedance (10:1) probe: This probe is also known as passive voltage probe. The basic function of this probe is to increase the input impedance and reduce the effective input capacitance of an oscilloscope.



The probe head uses a resistor and capacitor combination.

Active probe: The active probes are used for connecting fast rising and high frequency signals. These probes are very useful for small signal measurements as their attenuation factor is very small.

Current probe: This probe provides a method of inductively coupling the signal to the CRO input. The direct electrical connection between the test circuit and CRO is not necessary. This probe can be clamped around a wire carrying an electrical current without any physical contact to the probe.

Differential probes: It is a type of active probe. It has a two inputs, positive and negative. It has a separate ground lead and it drives single terminated 50  $\Omega$  cable to transmit its output to one oscilloscope channel.

4.

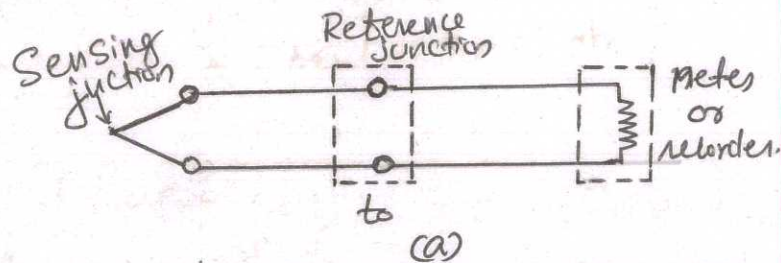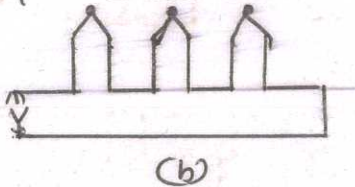

DB-2  
Exp 4  
2+4  
=6

6

A thermocouple is formed by joining two dissimilar metals. The junction is called the sensing or hot end. The other ends are called the reference or cold ends. When there is a raise in temperature between the cold end and hot end of the thermocouple, a voltage is produced which drives a current through the recorder or meter. The current produced is proportional to the temperature difference between hot and cold ends of the thermocouple as shown in fig (a). As the current indicated by the indicating instruments is proportional to the difference of temperature, these thermocouples are used for temperature sensing, heat flow and heat radiation detection.

When number of thermocouples are connected in series it is called a thermopile as shown in fig (b). Thermocouples are manufactured from different metal alloys. The usual operating temperature ranges from  $-270^{\circ}\text{C}$  to  $2700^{\circ}\text{C}$ . They are made in un-insulated wire form or may be incorporated in protective sheaths or probes. They are preferred in industrial furnaces and in measurement in cryogenic range because of the temperature range covered.


5. 1. The balance equation is independent of the magnitude of the input voltage or its source impedance.
2. The measurement accuracy is high as the measurement is done by comparing the unknown value with the standard value.
3. The accuracy is independent of the characteristics of a null detector and is dependent on the component value. 1x6 6 6
4. The balance equation is independent of the sensitivity of the null detector, the impedance of the detector or any impedance shunting the detector.
5. The balance condition remains unchanged if the source and detector are interchanged.
6. The bridge circuit can be used in the control circuit.

Sl. No.	open loop	closed loop
1.	Any change in output has no effect on the input	change in out, effect the input
2.	Output measurement is not required for operation of system	Output measurement is necessary
3.	Feedback element is absent	Feedback element is present
4.	Error detector is absent	Error detector is necessary
5.	It is inaccurate and unreliable	Highly accurate and reliable
6.	Highly sensitive to the disturbances	Less sensitive to the disturbances
7.	Simple construct and cheap	Complicated to design and hence costly
8.	Bandwidth is small	Bandwidth is large.

1x6 6 6

7. Telemetry is a system meant for collection of data from different remote locations and transfer the data to a centralized installation. Many electrical sensors will be used that perpetually measure the system operation. The different outputs of the individual sensors will be scanned at fixed intervals. They are multiplexed and transmitted through a suitable link to the centralized data collection centre. At the centralized data collection centre the signals are received. The data will be reconstructed into the required format. It will be de-multiplexed. Then the data will be distributed among reading and monitoring systems individually.

6 6 6

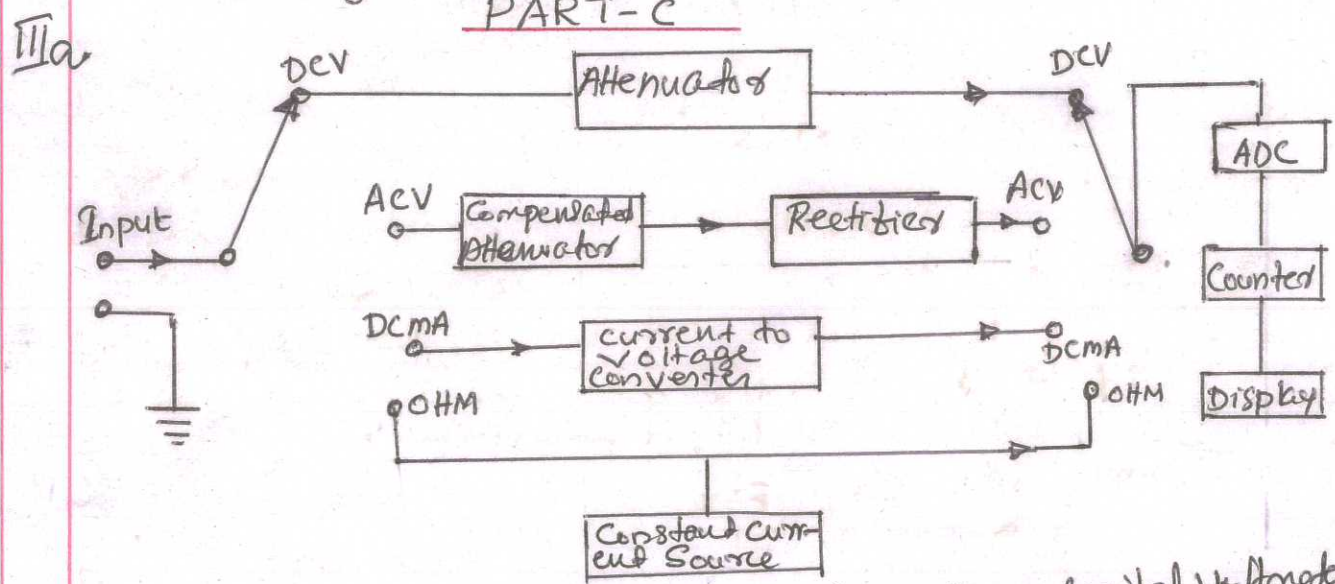


Digital multimeter (DMM) is basically a digital voltmeter and may be used for the measurement of voltage, current (dc or ac) and resistance. All quantities other than dc voltage are first converted into an equivalent dc voltage by some devices. For measurement of ac voltage the input voltage is converted into a dc voltage by means of a rectifier. A compensated attenuator is employed. Many manufacturers provide the same attenuator for both ac and dc measurement. For measurement of resistance, a constant current, depending on the range, supplied from a battery or a constant current source is passed through the resistance under measurement and the voltage developed across it is measured. The resistance value displayed in OHM. For measurement of current, the unknown current is passed through a precision resistor

bgs STA 9  
exp = 9  
4

in many Commercial DMM and the voltage developed across the resistor is measured. The current value is displayed in mA.

Sr No	Moving coil instruments	Moving iron Instruments
1.	It is used only for dc measurement	It can be used for both ac and dc measurement
2.	It is expensive	* It is cheapest
3.	They have a substandard accuracy	* They are very accurate
4.	The scale is uniform	* The scale is not uniform
5.	Power Consumption is very low.	* Power Consumption is moderate.
6.	Errors are less	* Errors are more.
7.	It is less robust	* It is more robust
8.	These are used in aircraft and aerospace instruments.	* These are used in laboratory and industrial instruments.

176 6 6

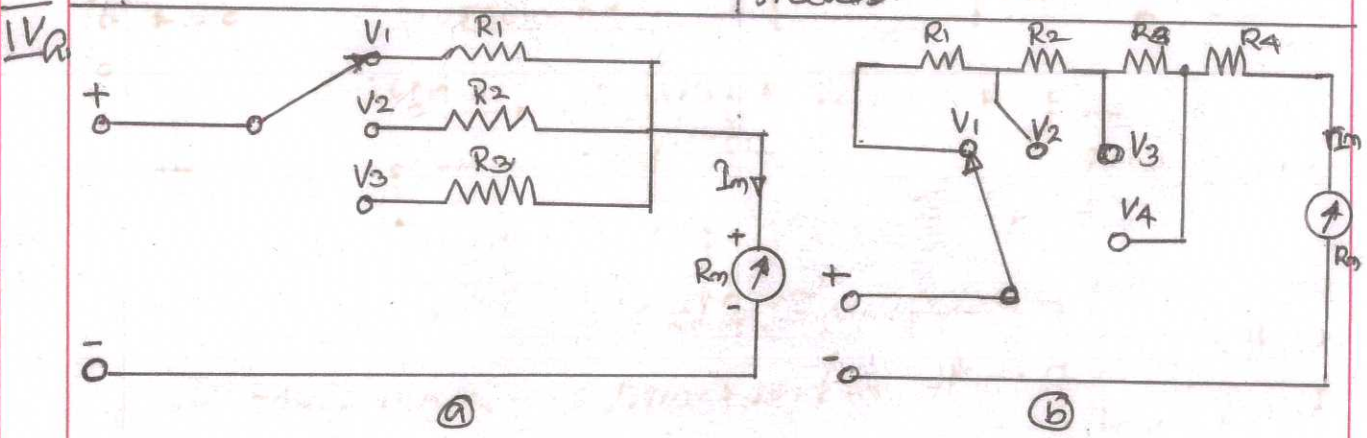

The basic moving system, often called the D'Arsonval movement, is called a basic meter.

The basic D'Arsonval movement can be converted into a multi-range voltmeter by connecting a number of resistors (multipliers) along with a range switch to provide a greater number of workable range.

Fig (a) shows a multi-range voltmeter a three position switch and three multipliers  $R_1, R_2, R_3$  for voltage values  $V_1, V_2$  and  $V_3$ .

$I_m$  = Full scale deflection current of the movement.

$R_m$  = Internal resistance of movement.

$\therefore R_1 = \frac{V_1}{I_m} - R_m$  for the voltage range  $V_1$

BS  
A  
CP  
A  
444  
=8  
8

$$R_2 = \frac{V_2}{I_m} - R_m \quad \text{for voltage range } V_2$$

$$R_3 = \frac{V_3}{I_m} - R_m \quad \text{for voltage range } V_3.$$

Fig (b) shows the modified form of multi-range voltmeter. In this arrangement, the multipliers are connected in a series string and the range selector selects the appropriate amount of resistance required in series with the movement. This arrangement is advantageous compared to the toggle, because all multiplier resistance except the first have the standard resistance value and also easily available in precision tolerances.

### b Specifications of Analog multimeter

AC/DC Voltage ranges: 0.5/1.5/3/5/12/15/30/50/120/150/300/500V

AC/DC Current ranges: 200mA/2/20/200mA/1A/10A

Resistance ranges: 0.2Ω to 100MΩ

Input impedance: 11MΩ for AC

Accuracy: ± 3%

Frequency response: 500 KHz

dB scale: 0dB corresponding to 1mW across 600Ω

Centre Zero scale: Available in all AC/DC Voltage range

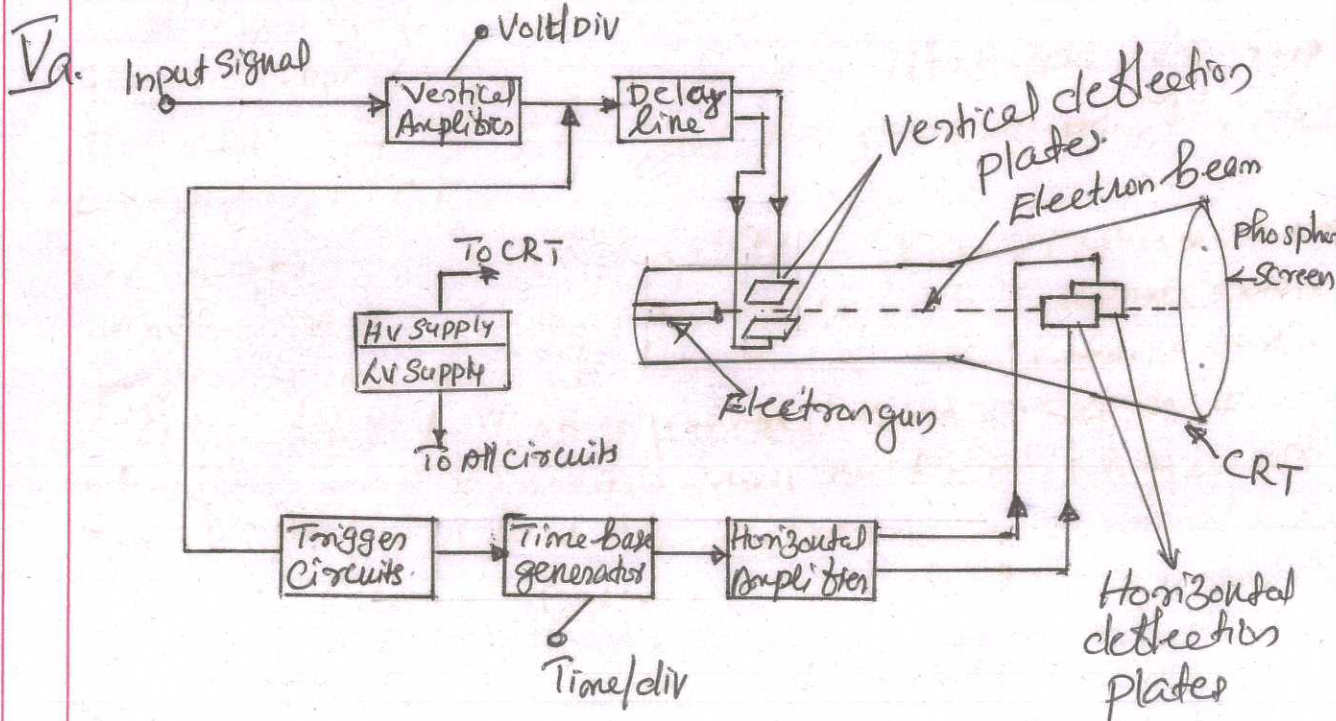


Fig 5 Exp 4 5th 9

As shown in the block diagram, having a main blocks are given below.

Cathode ray tube (CRT): The heart of CRO. The CRT produces sharply focussed beam of electron which strikes a fluorescent screen and produces a bright spot of light. This electron beam is made to move both horizontal and vertical direction to produce the waveform.

Vertical Amplifier: The signal to be observed on the screen of CRO is fed to the input of the amplifier. The output of the amplifier is fed to the vertical deflection plates of the CRT.

Delay line: It is used to delay the signal for some time in the vertical section.

Time-base generator: The time-base generator or sweep generator is used to generate the sawtooth voltage required to deflect the beam in the horizontal section. The rate of the sawtooth waveform is controlled by a control on the front panel of the CRO marked time/div.

Horizontal Amplifier: This amplifier either output of time-base generator is fed to the amplifier. The output of the amplifier is applied to horizontal deflection plates in push-pull form.


Trigger Circuits: The circuit produces a pulse called trigger pulse from the input waveform. This trigger pulse is used to start the time-base generator which in turn starts the horizontal sweep of the CRT spot from the left hand side of the screen.

Power Supply: This consists of a HV supply required for operating the CRT and LV power supply <sup>used</sup> for other circuits of CRO.

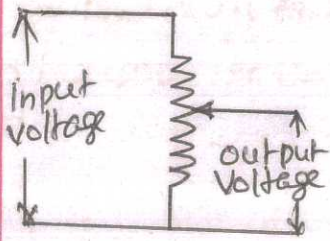
b) A potentiometric transducer is an electromechanical device. It is a passive transducer. It requires external power source for its functioning. It contains a resistance element, that is provided with a slider or wiper. The motion of the wiper may be translatory or rotational. Combination of translator and rotational motion leads to helical movement. Such potentiometers are called helipot. The translatory resistive element are linear devices, rotational resistive devices are circular. They are used for the measurement of angular

big  
3  
3+3  
3 26 6


displacement. Helipot are multi turn rotational devices. They can be used for either translatory or rotational motion.



Translatory type

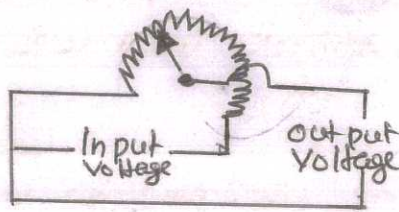


Rotational type

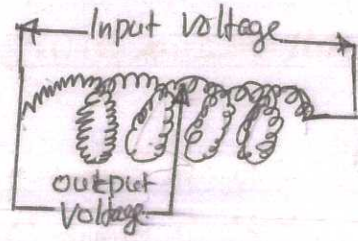

Helipot

VI  
a)

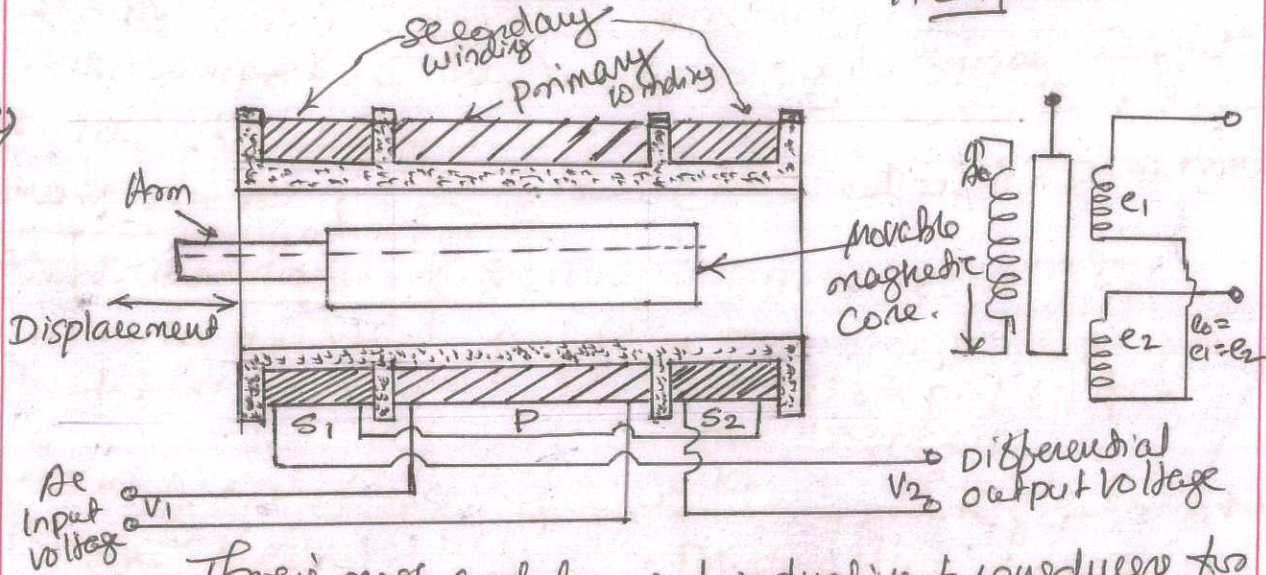

This is most widely used inductive transducer for translating linear motion into an electrical signal. The differential transformer is an electromechanical transducer which produces an electrical output proportional to the displacement of a movable core.

The LVDT is a differential transformer consisting of one primary winding P and two identical secondary windings S1 and S2 wound over hollow bobbins of non-magnetic and insulating materials. The secondary windings S1 and S2 are equal number of turns, are arranged concentrically and placed either side of the primary winding. A soft iron core, attached to the sensing element of which displacement is to be measured. The primary winding is connected to the ac source and secondary coils are connected in phase opposition. The voltage induced in the two secondary coils are dependent upon their respective induction with primary winding. This is governed by the position of the core. There exist a null position of the movable core when both secondary coils induce the same voltage i.e.,  $e_1 = e_2$ . Then  $e_0$  the output voltage is equal to zero. A slight movement of the core upwards from this position will produce  $V_{out}$ .

fig  
A  
exp 5  
AHS  
29  
9

tion in the coupling and  $e_1$  will be greater than  $e_2$ .

$\therefore e_0 = e_1 - e_2$  - will be non zero.

If the displacement takes place in the downward direction from the null position,  $e_2$  greater than  $e_1$   $\therefore e_0 = e_2 - e_1$


Advantages: ① Good linearity ② The resolution is infinite ③ High output ④ Good Sensitivity ⑤ low power consumption ⑥ Rugged in construction ⑦ low hysteresis

Disadvantages: - ① They are sensitive to stray magnetic fields shielding is required ② The receiving instrument must work on AC ③ It is affected by temperature.

b) $\frac{e_1}{e_0}$	Dual-trace CRO	Dual-beam CRO
1.	only one vertical amplifier is used	* Contains two separate vertical amplifiers for two channels.
2.	only one electron gun and one beam.	* Two separate electron guns produce two beams
3.	Two signals are switched to a single vertical amplifier	* Two signals are fed to two separate vertical amplifiers to get two separate images
4.	Cost is less	* Cost is more.
5.	Different display modes such as alternate, chopped, add etc. are possible	* Does not have many display modes; but well suited for simultaneous display of the widely different input signals.

4x  
15  
26 6 6

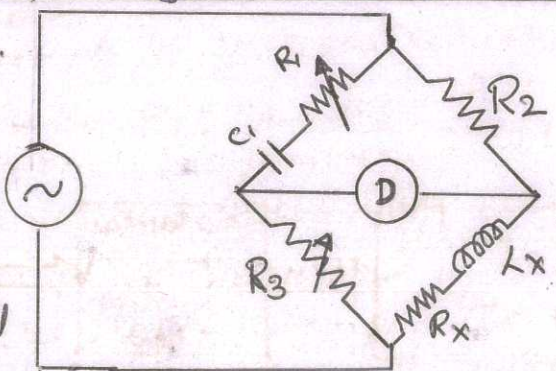VII  
a. Fig. shows the Hay's bridge. They differ from Maxwell's bridge by having a resistance  $R_1$  in series with a standard capacitor  $C_1$  instead of parallel. The unknown inductance  $L_x$  and its resistance parts are represented by  $L_x$  and  $R_x$  respectively and other two arms used capacitor  $C_1$  and variable resistance  $R_1$ . The other two arms have  $R_2$  &  $R_3$ .



At balance,  $Z_1 Z_x = Z_3 Z_2$  — (1)

Where,  $Z_1 = R_1 - j/\omega C_1$ ;  $Z_2 = R_2$ ,  $Z_3 = R_3$ ,  $Z_x = R_x + j\omega L_x$

Substituting values in equation no. 1 we get,

$$(R_1 - \frac{j}{\omega C_1})(R_x + j\omega L_x) = R_2 R_3$$

$$R_1 R_x + \frac{L_x}{C_1} - \frac{j R_x}{\omega C_1} + j\omega L_x R_1 = R_2 R_3 \quad \text{--- (2)}$$

Equating the real and imaginary terms we have

$$R_1 R_x + \frac{L_x}{C_1} = R_2 R_3 \quad \text{--- (3)}$$

$$\frac{R_x}{\omega C_1} = \omega L_x R_1 \quad \text{--- (4)}$$

$$\therefore R_x = \omega^2 L_x C_1 R_1 \quad \text{--- (5)}$$

Substituting  $R_x$  in equation (3)

$$R_1 (\omega^2 L_x C_1 R_1) + \frac{L_x}{C_1} = R_2 R_3$$

$$\omega^2 R_1^2 C_1 L_x + \frac{L_x}{C_1} = R_2 R_3$$

Multiplying both sides by  $C_1$  we get


$$\omega^2 R_1^2 C_1^2 L_x + L_x = R_2 R_3 C_1$$

$$\therefore L_x = \frac{R_2 R_3 C_1}{1 + \omega^2 R_1^2 C_1^2}$$

Substituting  $L_x$  in equ (5) we get,

$$\therefore R_x = \frac{\omega^2 C_1^2 R_1 R_2 R_3}{1 + \omega^2 R_1^2 C_1^2}$$

b)

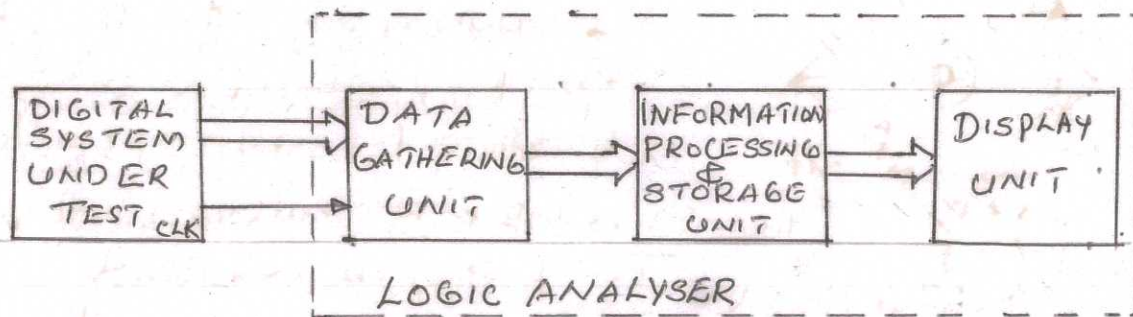

Logic analyser is developed to overcome the drawback of common oscilloscope. It operates on a slightly different principle than that of a oscilloscope. Because there are many signal lines

Q5  
2  
Cap  
2  
done  
↑  
2+2  
+4  
=8

in a digital system, the data is changing rapidly on each line, a logic analyzer must take a snapshot of the activities on the line and store the logic state of each signal in memory for each cycle of the system clock. The conditions under which the snapshot is taken are determined by triggering circuits, which can respond to various combinations of events.

The logic analyzer enable the activity of many digital signal points to be recorded simultaneously and then examined in details. The information is recorded with respect to a clock signal to determine whether they are HIGH or LOW with respect to a defined threshold voltage. This information is stored in memory and is then available for detailed analysis via logic analyzer's display. The clock signal can be internally or externally generated.

Fig. shows the block diagram of a typical logic analyzer. It has a data gathering unit, information processing and storage unit and a display unit. The data gathering unit has (1) a port slots for carrying data from the digital system under test to the logic analyzer and (2) a key pad. The key pad is used to enter commands and setup the parameters that the logic analyzer will use. The display unit is a CRT that displays the command menu for the operator and also displays the output data.

DS-3  
EXP  
A



3+4  
=7

7

VIII

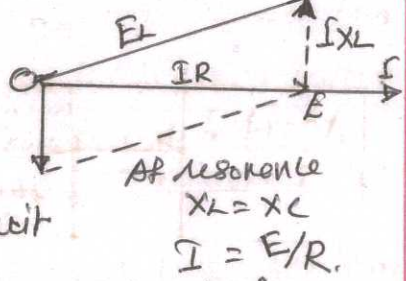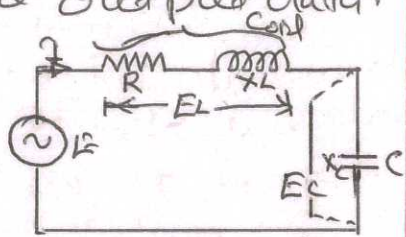a) The Q-meter is an instrument which is designed to measure of the electrical properties of the coils and capacitors by measuring the Q-value of an R-L-C circuit.

Working principle: It is based on the characteristics of a series circuit



These series resonant has a characteristic the voltage across the coil or capacitor is equal to the applied voltage times the Q factor of the circuit. The Q factor is called quality factor or storage factor. It is defined as the ratio of power stored in the element to the power dissipated in the element.

DS-4  
EXP  
A

4+4  
=8

8

The fixed voltage is applied to the circuit, a voltmeter across the capacitor can be calibrated to read Q directly. The voltage and current relationship of a series resonant circuit are shown in fig.


At resonance,  $X_L = X_C$ ;  $E_C = I X_C = I X_L$ ;  $E = IR$ .  
 where,  $E$  = applied voltage,  $I$  = circuit current

$E_C$  = voltage across the capacitor;  $X_C$  = Capacitive reactance

$X_L$  = inductive reactance;  $R$  = coil resistance.

The magnification of the circuit, by definition is  $Q$ , is given by,  $Q = \frac{X_L}{R} = \frac{X_C}{R} = \frac{E_C}{E}$

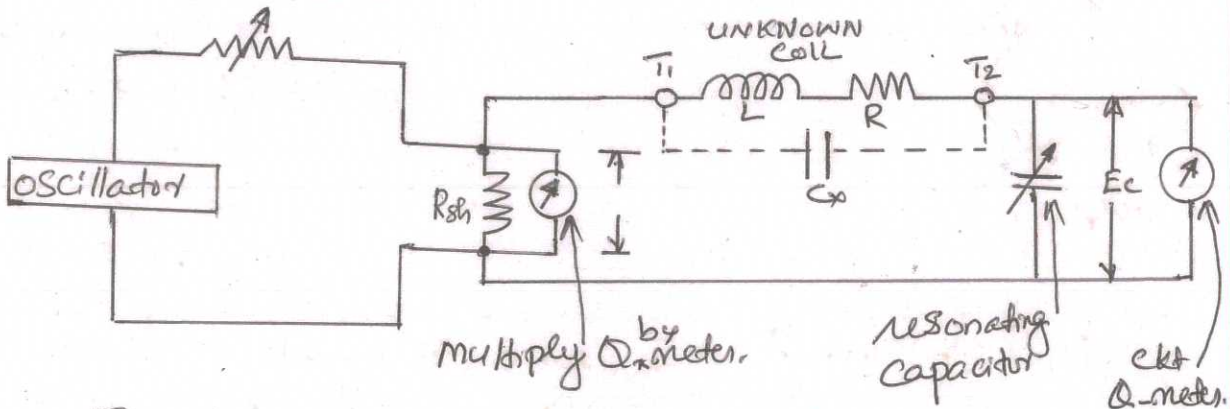Therefore, if  $E$  is maintained at constant and known voltage, a voltmeter connected across the capacitor can be calibrated directly in terms of the circuit  $Q$ .  
Practical Q-meter:



Q-meter circuit consists of a wide range of oscillator with frequency range from 50 KHz to 50 MHz. It delivers current to a low value shunt resistor  $R_{sh}$ . The value of the shunt is very low about  $0.02 \Omega$ . It introduces almost no resistance into the oscillatory circuit and it therefore represents a voltage source of magnitude  $E$  with a very small internal resistance. The voltage  $E$  across the shunt is measured with a thermocouple meter marked "multiple by  $Q$ ". The voltage across the variable capacitor  $E_C$  is measured with an electronic voltmeter whose scale is calibrated directly in  $Q$ -values.

Procedure: The unknown coil is connected to the test terminals of the instrument between  $T_1$  and  $T_2$ . The circuit is tuned to the resonance by setting oscillator to a given frequency and varying the internal resonating capacitor or by pre-setting the capacitor to a desired value and adjusting the frequency of the oscillator. The  $Q$  reading of the output meter must be multiplied by the index setting of the

"Multiple Q by" meter to obtain the actual Q value.  
 The indicated Q is the resonant reading on the "circuit Q" meter and called the circuit Q. The effective Q of the measured coil will be greater than the indicated Q. The difference is generally neglected.

The inductance of the coil can be calculated from the known values of frequency (f) and resonating capacitance (C)

$$X_L = X_C \text{ and } L = \frac{1}{(2\pi f)^2 C} \text{ henry}$$


b) Fig. shows to measure an unknown inductance in terms of a known capacitor. The use of standard arm offers the advantages of compactness and easy shielding. one arm has a resistance  $R_1$  in parallel with  $C_1$  and hence easier to write the balance equation using the admittance of arm 1 instead of the impedance.

At balance,

$$Z_1 Z_x = Z_2 Z_3$$

$$Z_x = \frac{Z_2 Z_3}{Z_1} = Z_2 Z_3 Y_1 \quad \text{--- (1)}$$

Where,  $Y_1 = \frac{1}{Z_1}$

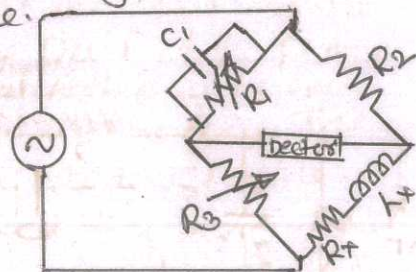

DS-3  
 Cor A  
 3+4  
 = 7

$Y_1 = \frac{1}{R_1} + j\omega C_1$ ;  $Z_2 = R_2$ ;  $Z_3 = R_3$  and  $Z_x = R_x + j\omega L_x$   
 substituting these values from equation - (1)


$$R_x + j\omega L_x = R_2 R_3 \left( \frac{1}{R_1} + j\omega C_1 \right)$$

$$= \frac{R_2 R_3}{R_1} + j\omega C_1 R_2 R_3$$

equating the real and imaginary terms we have,

$$\boxed{R_x = \frac{R_2 R_3}{R_1}} \text{ and } \boxed{L_x = C_1 R_2 R_3}$$

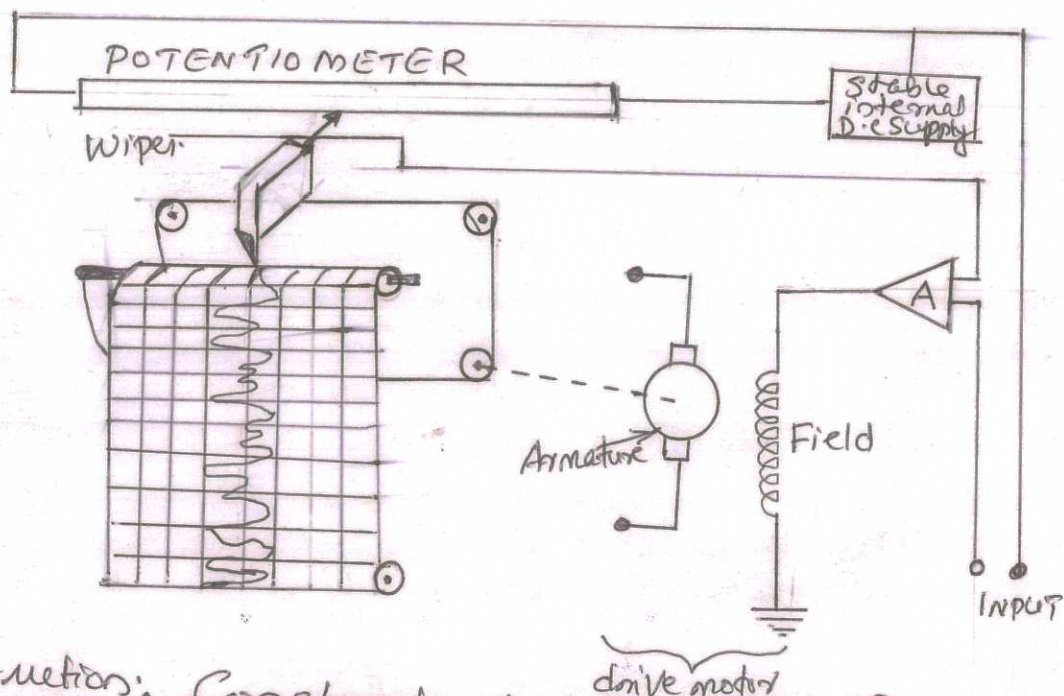ix a) The basic disadvantages of the galvanometer recorder is that having very low input impedance and sensitivity. The low input impedance creates a problem of loading. To overcome this, we can use an amplifier which provides high input impedance and reasonably high sensitivity, but accuracy is reduced. To overcome this problem, the input signal is compared with reference voltage.



BS-3  
exp 3+5  
5 = 8 8

Construction: Constructional details as shown in the block diagram, it can be seen that the input signal is applied to the amplifier in series with the part of the potentiometer. The potentiometer is supplied with a reference voltage derived from the internal power supply. The output of the internal power supply is made stable. The field coil of the motor is energised by the output of the amplifier. The output of the amplifier is the error signal. The wiper of the potentiometer is connected to the armature of the motor. The wiper carries a pen. The paper feed mechanism moves the paper with a constant speed.


Working: The difference in the put signal and reference potentiometric voltage produces the error signal. The error signal is amplified and it then energises the field coil of the d.c. motor. The error current either flows in the clockwise direction or anticlockwise direction depending on the voltage value. The motor turns such a direction that it reduces error signal to achieve balanced condition. As the error signal starts reducing, the motor slows down and stop completely when error become zero. Thus balanced condition is achieved. As the wiper of the potentiometer is driven by the motor's armature and a pen is arranged over the wiper, the pen executes motion in the direction of movement of the wiper. As the armature moves either direction depending on the error the pen moving in synchronism's direction records the waveform. The paper feed motor will be synchronized with power line frequency. Capillary

action of a recorder is defined as the process of establishing flow of info from the reservoir through the tubing and into the hollow of the pen.

- b) 1. It must acquire the necessary data at correct speed and at the correct time.
2. It must use all data efficiently to inform the operator about the state of the plant.
3. It must monitor the complete plant operation to maintain on-line optimum and safe operation
- A. It must provide an effective human communication system and able to identify problem areas, thereby minimizing unit availability and maximizing unit through put at minimum cost.
5. It must be able to collect summaries and store data for diagnosis of operation and record purpose
6. It must be able to compute unit performance indices on-line, real-time data.
7. It must be flexible and capable of being expanded to future requirements.
8. It must be reliable and not have a down time greater than 0.1 %

ix 7 7 7

Xo

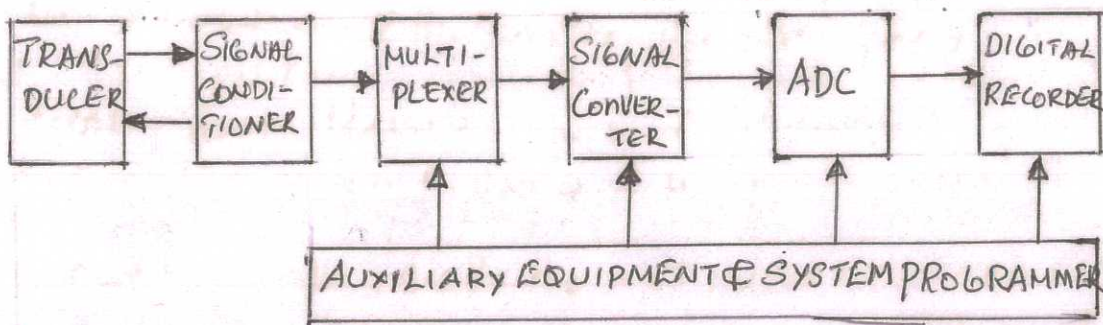

Analog DAS are used for measurement systems with wide bandwidths. But accuracy is less. So digital DAS which have high accuracy, low per channel cost and narrow bandwidths are designed.

The function of the digital DAS includes handling analog signals, making the measurement, converting and handling digital data, internal programming and control.

Digital DAS as shown in fig: Electrical quantities such as voltage, resistance and frequency may be measured directly. The signal conditioner includes the supporting circuitry for the transducers. This circuit may provide excitation power

balancing circuits and calibration elements and an example of this is a strain-gauge bridge lance and Power Supply Unit. The Scanner or multiplier accepts multiple analog inputs and sequentially connects them to one measuring instrument. The signal converter translates the analog signal to form acceptable by the A/D like an amplifier used for amplifying low-level voltage generated by thermocouples or strain-gauge. The output of the A/D may be displayed visually and is also available as voltage outputs discrete steps for further processing or recording on a digital recorder. The auxiliary section contains instrument for system programming and digital data processing such as linearizing and limit comparison. These functions may be performed by individual instruments or by a digital computer. The digital recorder records digital information on punched cards, perforated paper tape, magnetic tape, typewritten pages or a combination of these systems. Digital recorder may be preceded by a coupling unit that translates the digital information to the proper form for entry into particular digital recorder selected.

b) 9A  
 5 = 9 9

b)

S.No	Strip chart recorder	X-Y recorder.
1	Also known as X-t plotter	Also known as X-Y plotter
2	Input variable is plotted as a function of time	One input variable is plotted as a function of other
3	Paper is kept rotating	Paper is held stationary
A	Zero offset adjustment are not available	Zero adjustments are available.

Ax15  
 = 6 6 6