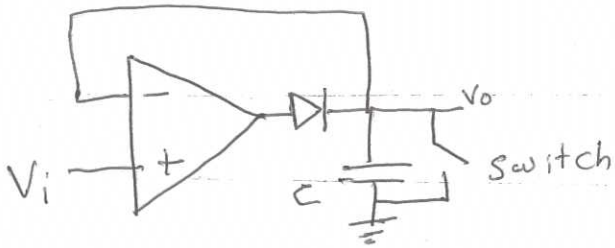
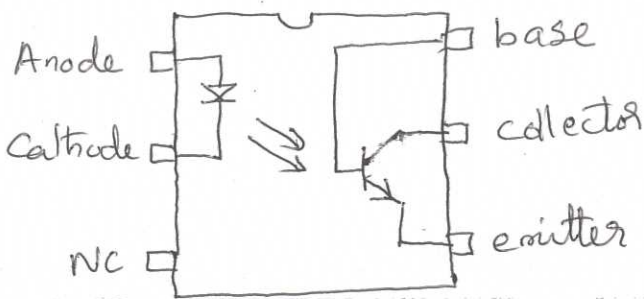




# SCHEME OF VALUATION


REV: 2015




COURSE TITLE: **Linear Integrated Circuits**


COURSE CODE: 4042

QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
I				
1.	<p>Slew rate is defined as maximum rate of change of output voltage caused by step input voltage</p>	2	2	
2.		2	2	
3	<p>pull-in time is defined as the total time taken by PLL to establish lock</p>	2	2	
4			2	
5)	<p>Astable multivibrator</p> <p><math>T = 0.69(R_A + 2R_B)C</math> - Asymmetrical or</p> <p><math>T = 0.69(R_A + R_B)C</math> - Symmetrical</p> <p>Monostable multivibrator</p> <p><math>T = 1.1RC</math></p>	1		
		1	2	10

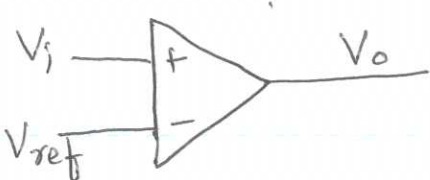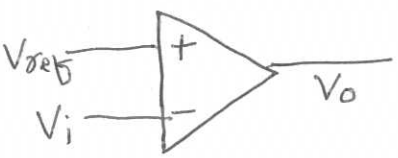Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
II				
1	<p>open loop gain = <math>\infty</math></p> <p>Input impedance = <math>\infty</math></p> <p>output impedance = 0</p> <p>Bandwidth = <math>\infty</math></p> <p>zero offset voltage</p> <p>Slew rate = <math>\infty</math></p> <p>CMRR = <math>\infty</math></p> <p>Input bias current = 0</p> <p>Input offset current = 0</p> <p style="text-align: right;">(Any six)</p>	1x6	6	
2	<p>Two types</p> <p>1) Non Inverting comparators</p> <div style="text-align: center; margin: 10px 0;">  </div> <p style="margin-left: 40px;"><math>V_i &gt; V_{ref} \quad V_o = +V_{sat}</math></p> <p style="margin-left: 40px;"><math>V_i &lt; V_{ref} \quad V_o = -V_{sat}</math></p> <p>2) Inverting comparators</p> <div style="text-align: center; margin: 10px 0;">  </div> <p style="margin-left: 40px;"><math>V_i &gt; V_{ref} \quad V_o = -V_{sat}</math></p> <p style="margin-left: 40px;"><math>V_i &lt; V_{ref} \quad V_o = +V_{sat}</math></p>	3		
		3	6	

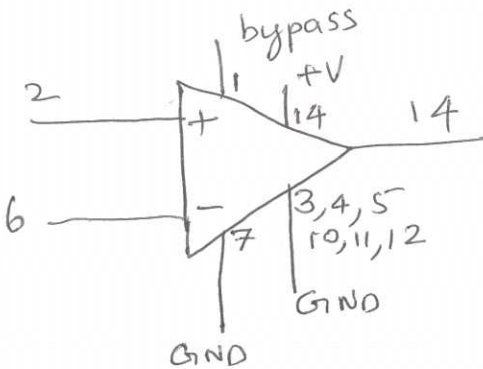Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
3	<p><u>LM380</u></p> <p>It is an audio power amplifier It supply large current to load such as speaker</p> <p><u>features</u></p> <p>fixed gain of 50, can be increased to 300 High Impedance Low distortion No need to use sepearate heat sink</p> 	4		
4	<p><u>Advantages of SMPS</u></p> <p>high efficiency small size Light weight Low power dissipation (Any 3)</p> <p><u>Disadvantages of SMPS</u></p> <p>Erreater complexity in circuit simple design have power factor Costly It can cause harmonic distortion (Any 3)</p>	2	6	
		3		
		3	6	

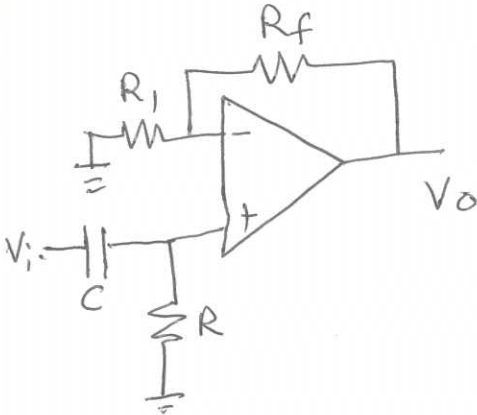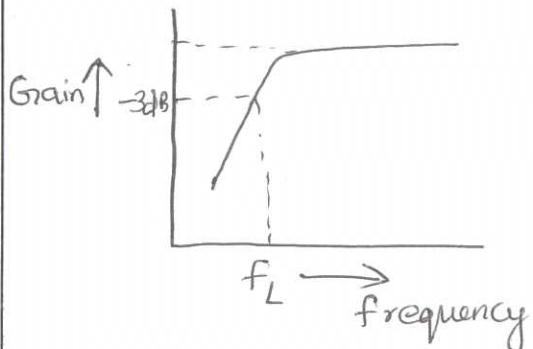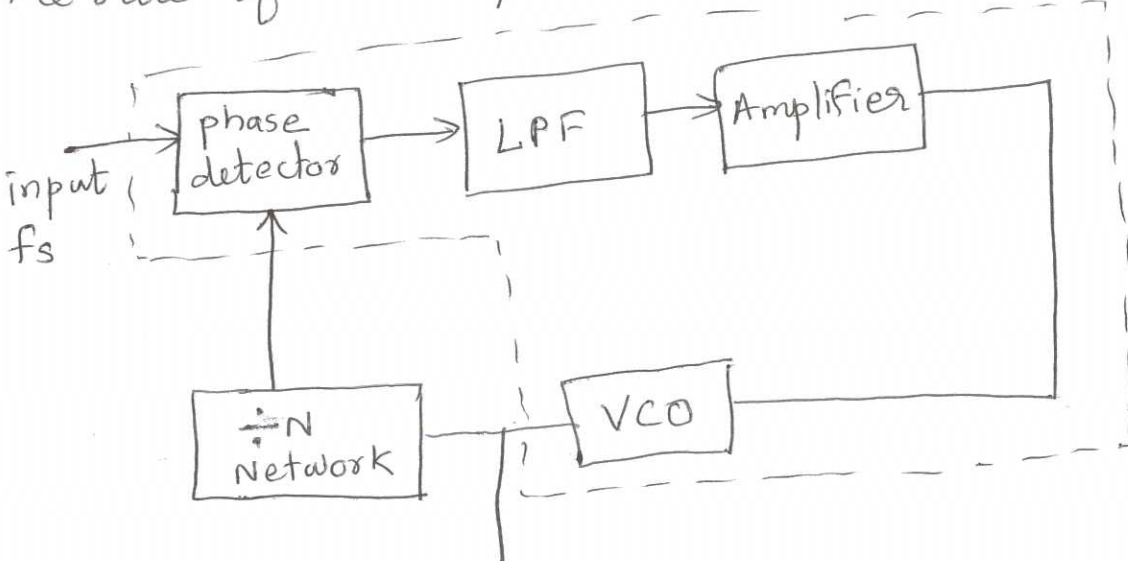Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
5	  <p>It blocks low frequencies <math>\text{Gain} = 1 + \frac{R_f}{R_1}</math>  <math>f_L = \frac{1}{2\pi RC}</math>. Below <math>f_L</math> gain increases at the rate of 20dB/decade</p>	2		
6	 <p style="text-align: center;"><math>f_o = Nf_s</math></p> <p>Frequency divider divides the frequency by a factor N. Since divided frequency is in lock with input frequency, VCO is running at the multiple of input frequency</p>	4		
		2	6	

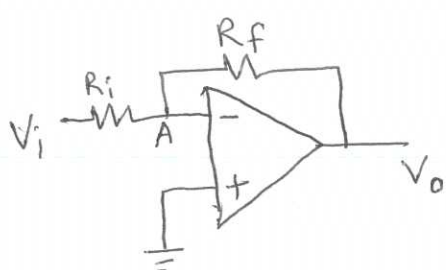Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
7	<p>LM 723 features</p> <ol style="list-style-type: none"> <li>1) Maximum input voltage = 40V</li> <li>2) output voltage can be adjusted from 2V to 37V</li> <li>3) It provides upto 150mA o/p current</li> <li>4) Output current can be boosted upto 10A</li> <li>5) It can be used as a switching or linear regulator</li> <li>6) both positive and negative voltage can be obtained</li> </ol>		1x6	6
III a)	 <p style="margin-top: 20px;">Voltage at A, <math>V_A = 0V</math></p> <p>Applying KVL at A</p> $-\frac{V_A - V_i}{R_i} + \frac{V_A - V_o}{R_f} = 0$ $\frac{V_o}{V_i} = -\frac{R_f}{R_i}$	3	4	7

# SCHEME OF VALUATION


REV: 2015

COURSE TITLE: Linear Integrated Circuits

COURSE CODE: 4042

QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
--------	-------------------	----------------	-----------	-------

III  
b

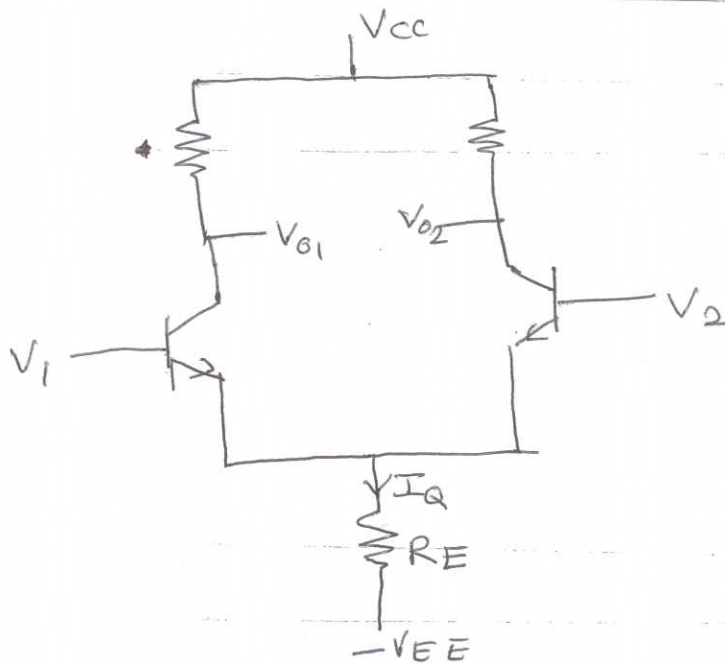

When  $V_1 = V_2 = V_{CM}$  (common mode voltage)

$$V_{01} = V_{02} = V_{CC} - \alpha \frac{I_Q}{2} R_E$$

Therefore the difference between the collector voltages  $V_{01} - V_{02} = 0V$

When  $V_1 = 1V$   $V_2 = 0V$

transistor  $Q_1$  will conduct  $Q_2$  is OFF

$$V_{01} = V_{CC} - \alpha I_Q R_E \quad V_{02} = V_{EE}$$

4


4 8 15

Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
----------	-------------------	----------------	-----------	-------

IV

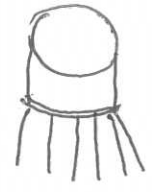a) 1) metal can package


chip is enclosed in metal case  
It is good for power amplifiers because of good heat dissipation capability



2

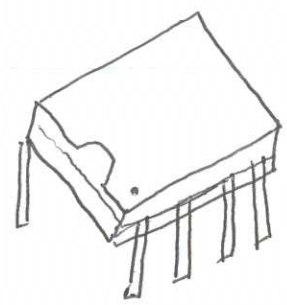2) Dual in line package (DIP)


chip is mounted inside plastic or ceramic case.



3

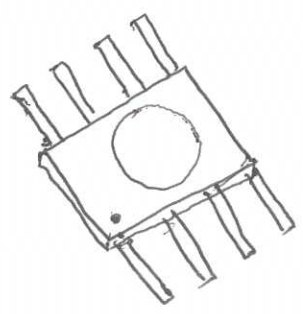3) flat package.

chip is enclosed in rectangular ceramic case




2

7

Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
----------	-------------------	----------------	-----------	-------

b)

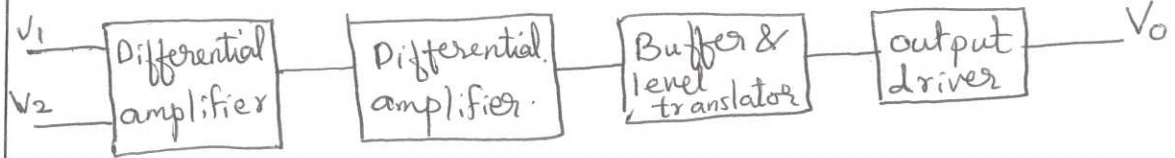

4


Differential amplifier provides high gain and high input impedance. Buffer is an emitter follower circuit whose input impedance is high. Level translator adjust the dc voltage, so that output voltage is zero for zero input voltages. Output driver provides low output impedance and increases the current supplying capability.

4

8

15

a)

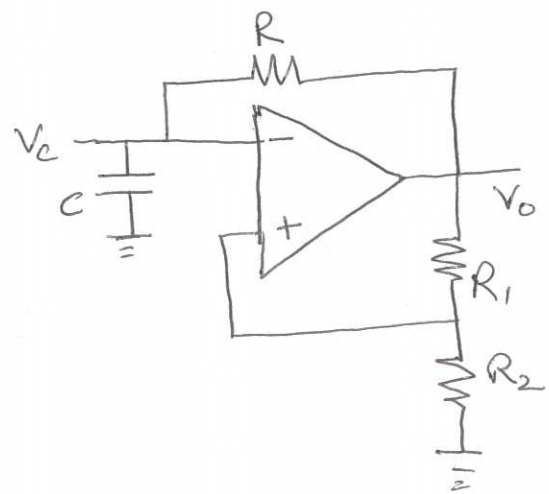

3


Qst.  
No.

Scoring Indicator

Split up  
score

Sub  
Total

Total

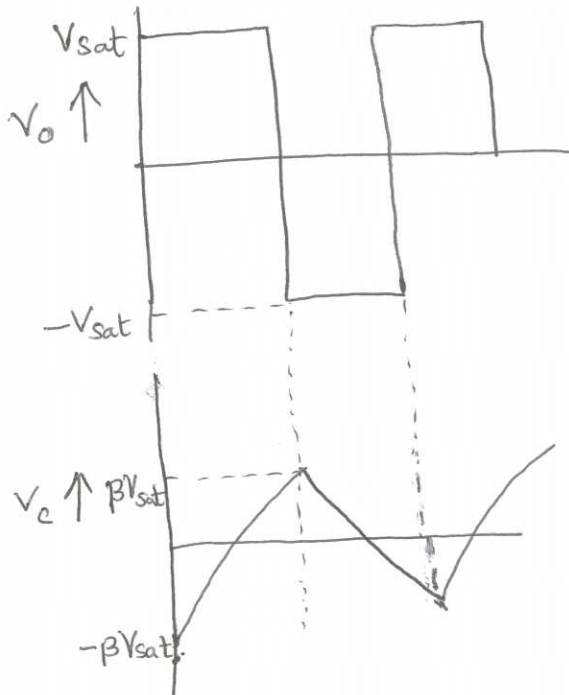

$$\beta = \frac{R_2}{R_1 + R_2}$$

when output voltage is  $V_{sat}$  capacitor charges towards  $+V_{sat}$  and when voltage across capacitor is just greater than  $\beta V_{sat}$  output switches to  $-V_{sat}$

Now the capacitor discharges and when the voltage across capacitor reaches just below  $-\beta V_{sat}$  output switches back to  $+V_{sat}$ . This cycle repeats


2

3

8


Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
----------	-------------------	----------------	-----------	-------

b)

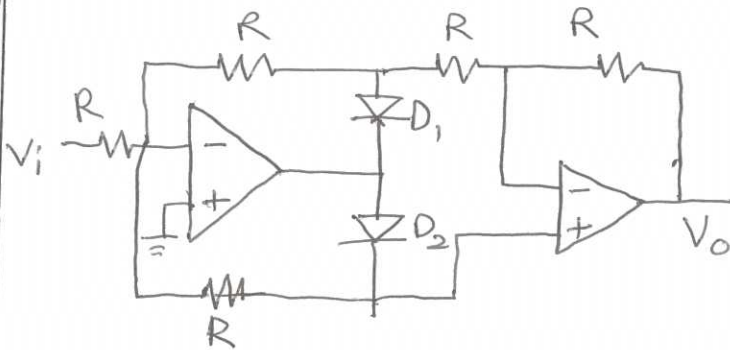


For positive input voltage  $D_1$  is ON and  $D_2$  is off.  $V_o = V_i$

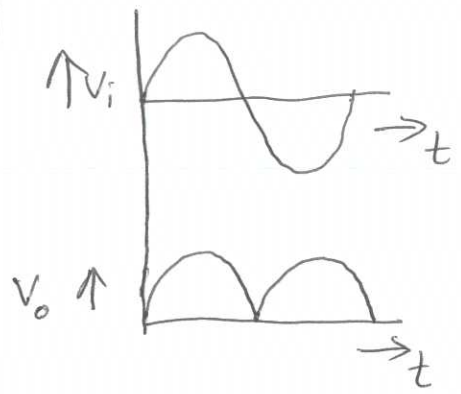For negative input voltage  $D_1$  is OFF and  $D_2$  is ON.  $V_o = -V_i$





V<sub>i</sub>

V to I converter

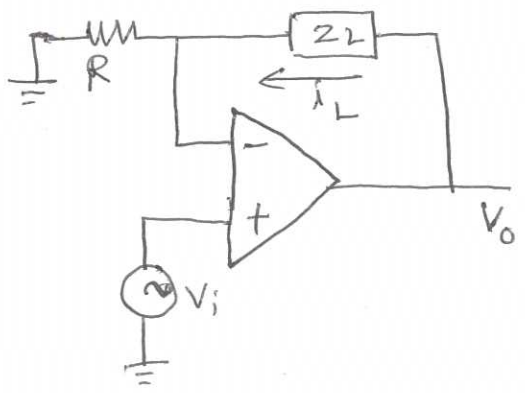

3

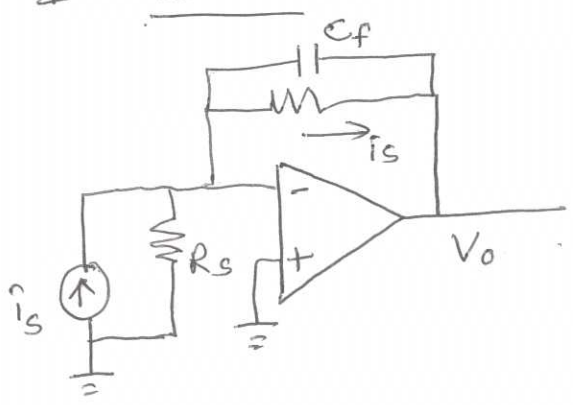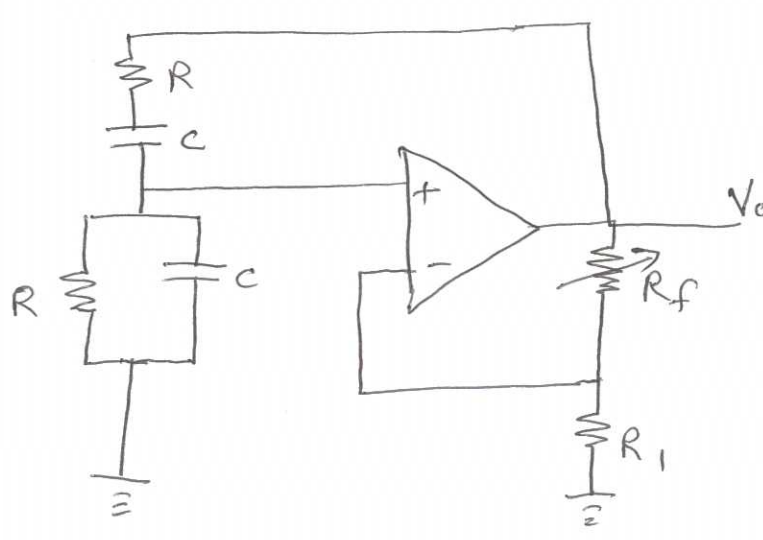Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
	<p>Voltage signal is converted to proportional output current</p> $i_L = \frac{V_i}{R}$	1		
b	<p><u>I to V Converter</u></p> 	3		
	<p>Current signal is converted to proportional output voltage.</p> $V_o = - i_s R_f$	1	8	
b)	<p><u>Wien bridge Oscillator</u></p> 	4		

Qst. No.	Scoring Indicator	Split up score	Sub Total	Total
----------	-------------------	----------------	-----------	-------


Audio frequency oscillator of high stability and simplicity. The feedback signal in this circuit is connected to non inverting input terminal so that op-amp is working as non inverting amplifier. Feedback network neednot provide any phase shift.

Frequency of oscillation =  $\frac{1}{2\pi RC}$

feedback factor  $\beta = \frac{1}{3}$ . For sustained oscillation amplifiers should have gain of 3

3 7 15

VIII  
a)

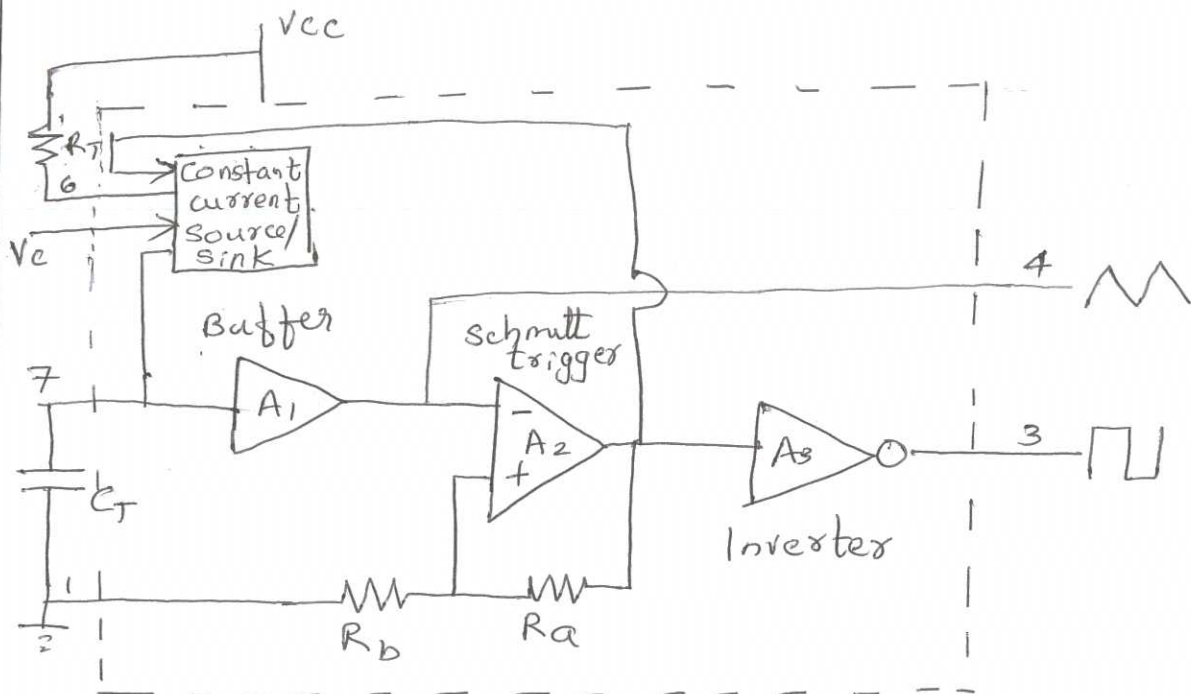

5

# SCHEME OF VALUATION

REV: 2015

COURSE TITLE: **Linear Integrated Circuits**

COURSE CODE: 4042

QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
	<p>Timing capacitor <math>C_T</math> is charged or discharged by constant current source/sink. The amount of current can be controlled by changing the voltage, <math>V_C</math> or by changing the timing capacitor, <math>R_T</math>. Since source and sink currents are equal capacitor charges and discharges for the same amount of time. This gives triangular wave. The square wave is obtained by using Schmitt trigger. Inverter is basically a current amplifier to drive the load.</p>	5	10	
b)	<p>Features of 555</p> <ol style="list-style-type: none"> <li>1) It operates on 5V to 18V</li> <li>2) It has adjustable duty cycle.</li> <li>3) Timing is from microsecond to hours</li> <li>4) It has high current output</li> <li>5) It can source or sink 200mA</li> <li>6) output can drive TTL (Any 5)</li> </ol>	5	5	15

# SCHEME OF VALUATION





REV: 2015

COURSE TITLE: Linear Integrated Circuits

COURSE CODE: 4042

QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
--------	-------------------	----------------	-----------	-------

VIII  
a)

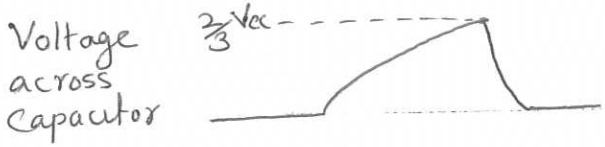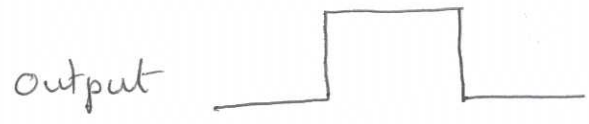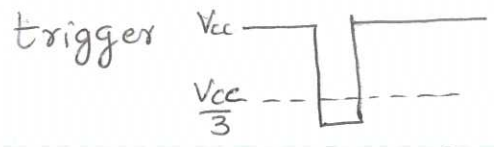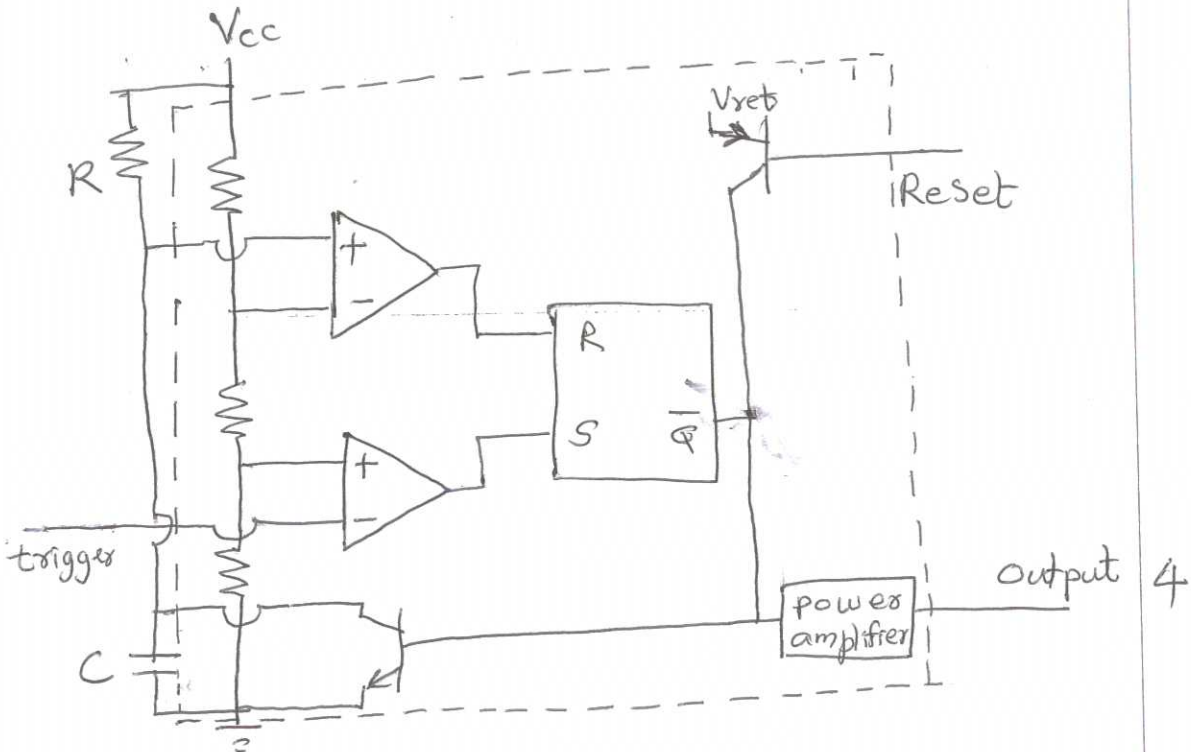

In stable state output is low  
 Initially  $S=R=0$ , when trigger voltage is less than  $\frac{V_{cc}}{3}$  output of lower comparator becomes high  
 $S=1$   $R=0$   $\bar{Q}=0$  ie, output is high

4

2

# SCHEME OF VALUATION

REV: 2015

COURSE TITLE: **Linear Integrated Circuits**

COURSE CODE: 4042

QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
	<p>Capacitor charges through resistor R when voltage across capacitor becomes greater than <math>\frac{2}{3}V_{CC}</math>. output of the upper comparator becomes high.</p> <p>when <math>S=0</math> <math>R=1</math>, <math>\bar{Q}=1</math> then output is low</p>	4		10
b)	<p>Electrical characteristics of PLL</p> <ol style="list-style-type: none"> <li>1) Operating frequency range 0.001Hz to 500kHz</li> <li>2) operating voltage range <math>\pm 6V</math> to <math>\pm 12V</math></li> <li>3) Input Impedance <math>10k\Omega</math></li> <li>4) o/p sink current 1mA</li> <li>5) o/p source current 10mA</li> <li>6) Bandwidth adjustment range <math>&lt; \pm 1\%</math> to <math>\pm 6\%</math></li> <li>7) triangular wave amplitude <math>2.4V_{pp}</math> at <math>\pm 6V</math></li> <li>8) Square wave amplitude <math>5.4V_{pp}</math> at <math>\pm 6V</math></li> <li>9) Drift in VCO centre frequency with temperature <math>-300ppm/^\circ C</math></li> <li>10) Drift in VCO centre frequency with supply voltage <math>-1.5\%/V_{max}</math></li> </ol> <p style="text-align: center;">(Any five)</p>	5	5	15

# SCHEME OF VALUATION

REV: 2015	COURSE TITLE: Linear Integrated Circuits	COURSE CODE: 4042		
QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
1X a)	<pre> graph LR     A[Input ac] --&gt; B[Input rectifier and filter]     B --&gt; C[Inverter Chopper]     C --&gt; D[output transformer]     D --&gt; E[output rectifier and filter]     E --&gt; F[dc]     G[chopper controller] --&gt; C     G --&gt; E             </pre>	4		
	<p>Input ac signal is rectified and filtered. The unregulated dc signal is fed to inverter section. It consists of fast switching devices which converts the signal to high frequency pulses (20kHz). output transformer step up or step down the signal to required level. The signal is again rectified and filtered to produce required dc voltage.</p>	4	8	

# SCHEME OF VALUATION


REV: 2015

COURSE TITLE: **Linear Integrated Circuits**

COURSE CODE: 4042

QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
--------	-------------------	----------------	-----------	-------

b)

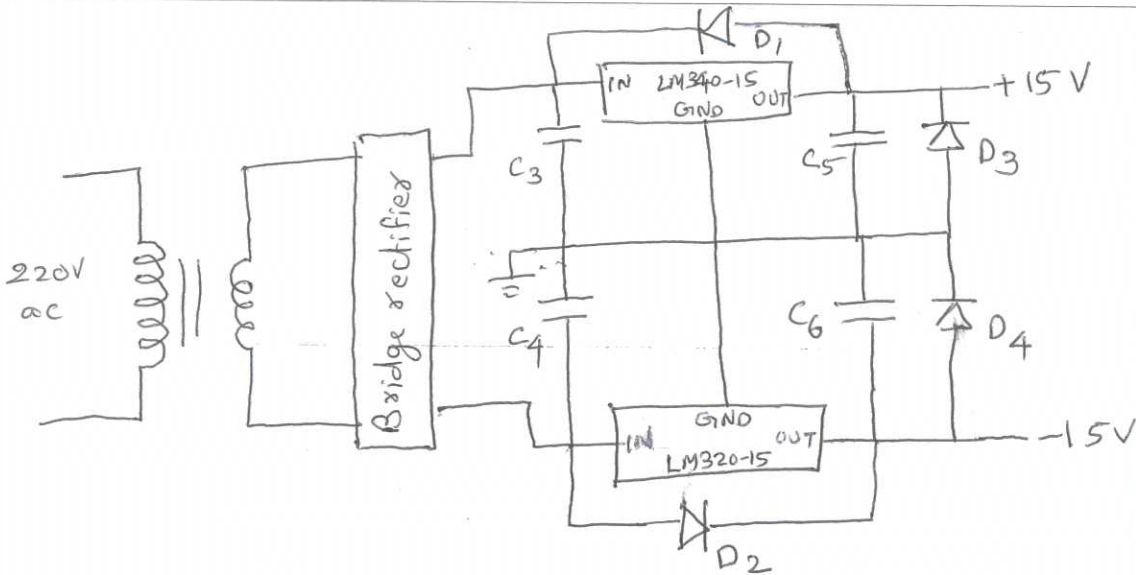

4

220V ac signal is step down using step down transformer. The signal is then rectified and filtered. LM340-15 is a +15V regulator. LM320-15 is a -15V regulator. Diodes  $D_1$  and  $D_2$  in the circuit protect the regulator against short circuit occurring at its input terminals. Diodes  $D_3$  and  $D_4$  provide protection against the situation when both of the regulators may not turn on simultaneously.

3 7 15

# SCHEME OF VALUATION

REV: 2015


COURSE TITLE: Linear Integrated Circuits

COURSE CODE: 4042

QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
X a)	<p>Low voltage regulator using LM723</p> 			
	<p>Regulated o/p voltage from 2V to 7V can be obtained.</p> $V_o = 7.15 \frac{R_2}{R_1 + R_2}$ $R_3 = R_1 \parallel R_2$ <p>Difference between voltage at the non inverting terminal and output voltage is amplified by the error amplifier. Output of the error amplifier drives the transistor, Q<sub>1</sub>. If output goes low voltage at the inverting terminal becomes less. This makes output of the error amplifier to become more positive. Thus output voltage is increased. Similarly any increase in load voltage gets regulated.</p>	6		
			4	10

X  
a)

Low voltage regulator using LM723

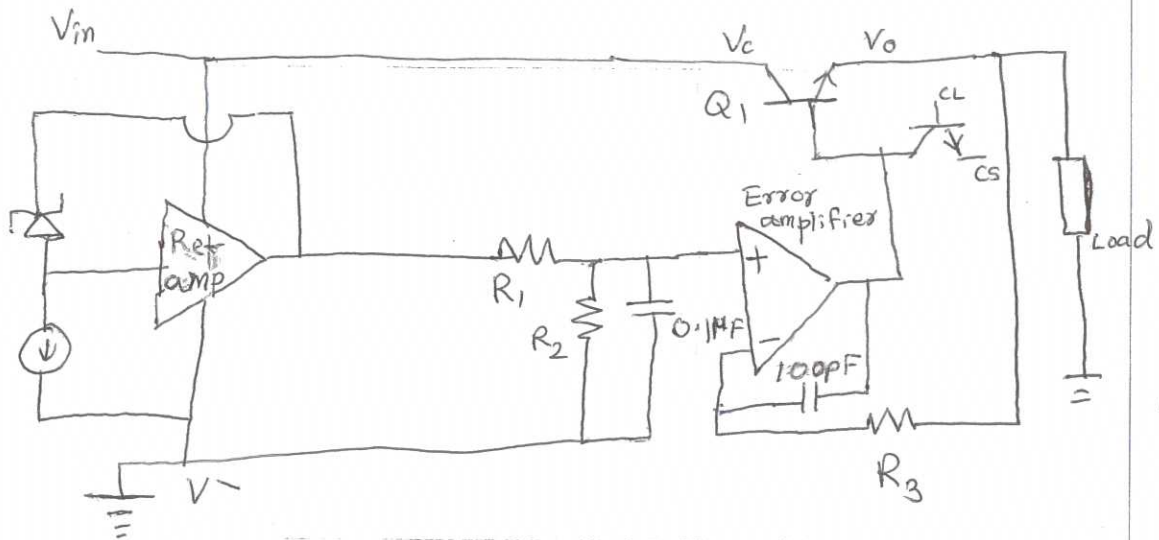

Regulated o/p voltage from 2V to 7V can be obtained.

$$V_o = 7.15 \frac{R_2}{R_1 + R_2}$$

$$R_3 = R_1 \parallel R_2$$


Difference between voltage at the non inverting terminal and output voltage is amplified by the error amplifier. Output of the error amplifier drives the transistor, Q<sub>1</sub>. If output goes low voltage at the inverting terminal becomes less. This makes output of the error amplifier to become more positive. Thus output voltage is increased. Similarly any increase in load voltage gets regulated.

# SCHEME OF VALUATION

REV: 2015

COURSE TITLE: Linear Integrated Circuits

COURSE CODE: 4042

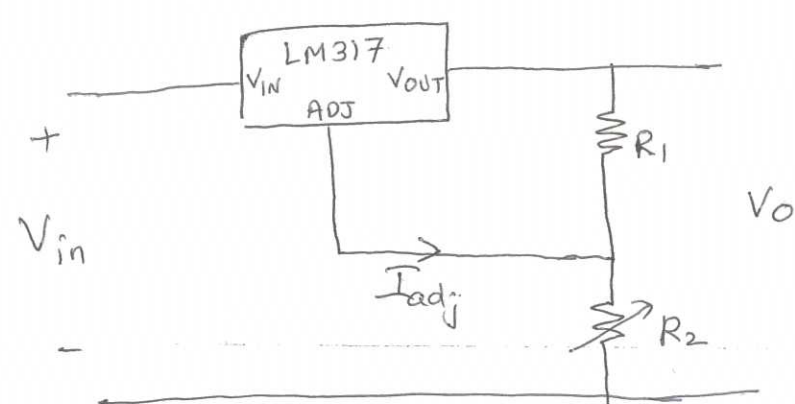QN NO.	SCORING INDICATOR	SPLIT UP SCORE	SUB TOTAL	TOTAL
b)	<p>LM317</p>  <p style="text-align: center;"> <math display="block">V_o = V_{REF} \left( 1 + \frac{R_2}{R_1} \right) + I_{adj} R_2</math> </p> <p>Its output voltage is from 1.25V to 37V By varying <math>R_2</math> output voltage can be varied</p>	3	2	5
			15	